

**B.Tech. – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

Term-End Examination

December, 2016

00093

BIELE-011 : DIGITAL SYSTEM DESIGN

Time : 3 hours

Maximum Marks : 70

Note : Attempt any **seven** questions. All questions carry equal marks. Use of scientific calculator is allowed.

1. Draw the logic diagram of a 4-bit look ahead carry adder and calculate the speed-up compared to a 4-bit binary ripple adder. 10

2. Reduce the state diagram shown in Figure 1 and also write the reduced state table. Consider the input sequence as "01010110100" starting from the initial condition '0'. 10

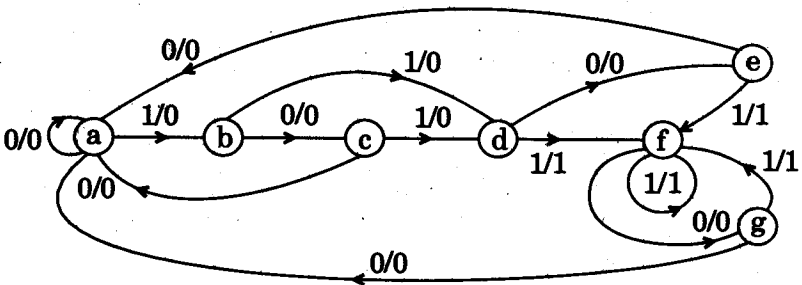


Figure 1

3. Design the controller whose state diagram is shown in Figure 2. Write the RTL model of the controller. 10

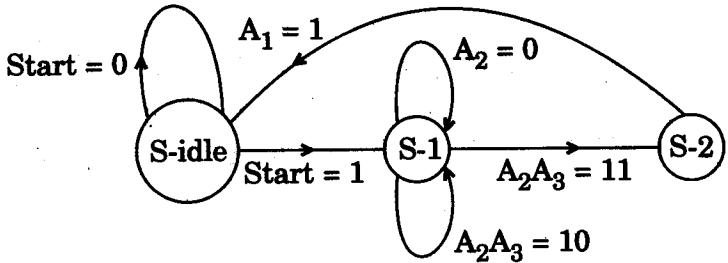


Figure 2

4. Implement the Boolean function

$$F(A, B, C, D) = \sum m(0, 2, 5, 7, 11, 14)$$
and

$$P(A, B, C, D) = \prod M(1, 4, 5, 7, 9, 12, 15)$$
with multiplexer. 10
5. Write the working principle of ROM matrix for implementing a truth table of a full subtractor. 10
6. (a) Differentiate between Synchronous state machine and Asynchronous state machine. 5
- (b) Design a Mod-6 up counter using J-K flip-flop. 5

7. Explain the types of operators in VHDL design. Write a program for a 4-bit binary to BCD conversion using data flow model. 10
8. Draw a multilevel NOR and multilevel NAND gate circuit to implement the Boolean function $F(A, B, C, D, E) = (\overline{A}B + C\overline{D})E + B\overline{C} (A + B)$. 10
9. Write the data flow description for a 4-bit comparator. The output of the comparator is '1' when both the inputs are unequal and is '0' for equal input. 10
10. Design a logic circuit that controls an elevator in a four-storied building. The circuit has two inputs for user to indicate the desired floor to reach. The lift starts moving when start input = 1. M is an output signal that indicates if the desired floor is reached (i.e., $M = 1$) and stops the lift for opening of gate. 'M' remains in low state (i.e., '0'), when the lift is moving. F_1 and F_2 are two outputs to show the floor level that the lift has reached. 10
-