

**B.Tech. - VIEP - ELECTRONICS AND  
COMMUNICATION ENGINEERING  
(BTECVI)**

**Term-End Examination**

**December, 2016**

00953


**BIELE-012 : ELECTRONIC SWITCHING CIRCUITS**

*Time : 3 hours*

*Maximum Marks : 70*

*Note : Attempt any seven questions. All questions carry equal marks. Assume missing data, if any. Use of scientific calculator is permitted.*

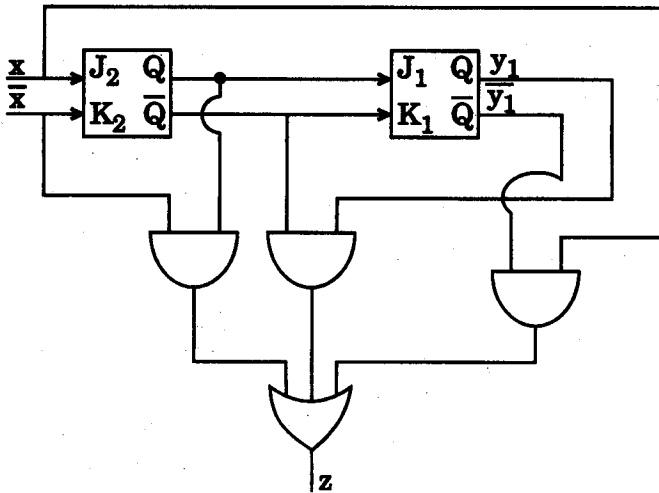1. Design a 3-bit up-down counter with a control input P such that when  $P = 1$ , it counts up and when  $P = 0$ , it counts down. 10
2. Analyze the synchronous circuit shown below :



(a) Write down the excitation and output functions.

(b) Form the excitation table and state table. 10

3. Design a modulo-8 counter which counts in the way given below. Use JK flip-flops in your realization. 10

<i>Decimal</i>	<i>Gray code (count sequence)</i>
0	000
1	001
2	011
3	010
4	110
5	111
6	101
7	100

4. The output  $z$  of a fundamental-mode two-input sequential circuit is to change from 0 to 1 only when  $x_2$  changes from 0 to 1, while  $x_1 = 1$ . The output is to change from 1 to 0 only when  $x_1$  changes from 1 to 0, while  $x_2 = 1$ .

(a) Find a minimum row reduced flow table.

(b) Write a set of hazard-free excitation and output equations. 10

5. A sequential circuit has two pulse inputs  $x_1$  and  $x_2$ . The output of the circuit becomes '1' when one or more consecutive  $x_1$  pulses are followed by two  $x_2$  pulses. The output then remains '1' for all subsequent  $x_2$  pulses until all  $x$  pulses occur.
- (a) Derive a minimal state table.
  - (b) Synthesize the circuit using set-reset flip-flops. 10
6. Explain the design of hazard-free combinational circuit and the design of hazard-free asynchronous circuit. 10
7. What are the different types of hazards ? Explain how these can be avoided. 10
8. Explain the synthesis of symmetric functions with the help of a suitable example. 10
9. Write short notes on any *two* of the following : 2×5=10
- (a) Generation of Spikes
  - (b) Relay Contents
  - (c) Conversion of Mealy Circuit to Moore Circuit
-