

**DECVI / DELVI / DCSVI / ACECVI / ACELVI /
ACCSVI**

Term-End Examination

December, 2016

00923

OIEE-001 : BASICS OF ELECTRICAL ENGINEERING

Time : 2 hours

Maximum Marks : 70


Note : Attempt any five questions. Question no. 1 is compulsory.

State whether the following statements are True or False :

7×2=14

1. (a) The resistance of a conductor increases, if its area of cross-section increases. [T/F]
- (b) Three resistances of $R \Omega$ each are connected in delta. Its equivalent star will comprise resistance of value $R/3$ each. [T/F]
- (c) The superposition theorem is applicable to only linear circuits. [T/F]
- (d) Magnetic flux density (B) is the ratio of cross-sectional area (A) to the magnetic flux (ϕ). [T/F]
- (e) The power factor of a purely resistive circuit is unity. [T/F]
- (f) In case of 3-phase Δ connected circuit, the total power is given by $\sqrt{3} V_L I_L \cos \phi$. [T/F]
- (g) The unit of electrical energy is kW. [T/F]

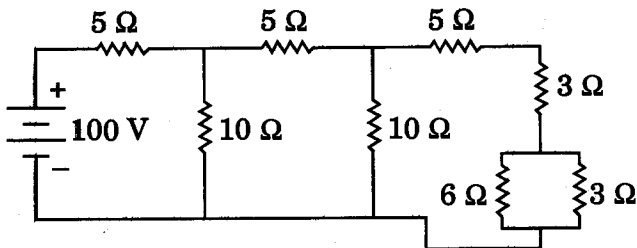2. (a) Define power factor. Explain the concept of power triangle with the help of power factor. 7
- (b) Calculate the value of form factor of a half wave rectified waveform. 7
3. (a) Derive an expression for the half cycle average value for sinusoidal current $i(t) = I_m \sin \omega t$. 7
- (b) In the circuit shown, determine :
 (i) the current supplied by the 100 V source, and (ii) the voltage across the 6 Ω resistor. 7



4. (a) State and explain Kirchhoff's voltage and current laws. 7
- (b) Compare primary and secondary cells. 7
5. (a) Derive the relations for conversion from delta to star connection for three-phase impedance. 7
- (b) State and explain superposition theorem with the help of a suitable example. 7

6. (a) A coil with 250 turns carries a current of 2 A, and produces a flux of 0.3 mWb. When this current is reduced to zero in 2 ms, the voltage induced in a nearby coil is 60 volts. Calculate (i) the self-inductance of each coil, and (ii) mutual inductance of coils. Assume coefficient of coupling = 0.7. 8
- (b) Give the comparison between electric and magnetic circuits. 6
7. Write short notes on any *four* of the following : $4 \times 3 \frac{1}{2} = 14$
- (a) Advantages of 3- ϕ over 1- ϕ system
 - (b) Reluctance
 - (c) Lenz's Law
 - (d) Hysteresis Loop
 - (e) Fleming's Right-Hand Rule
 - (f) Series Resonance
-