

**B.Tech. Civil (Construction Management) /  
B.Tech. Civil (Water Resources Engineering)**

**Term-End Examination**

**December, 2017**

00508

**ET-202(B) : PRINCIPLES OF ELECTRICAL  
SCIENCES**

*Time : 3 hours*

*Maximum Marks : 70*

---

*Note : Attempt any five questions. Use of scientific calculator is allowed. Missing data may be suitably assumed.*

---

---

1. (a) Discuss the following : 5×2=10
- (i) Kirchhoff's Voltage Law (KVL)
  - (ii) Maximum power transfer theorem
  - (iii) Power factor
  - (iv) Merits of 3-phase system
  - (v) Feedback system

- (b) Find the equivalent resistance ( $R_{AB}$ ) shown in Figure 1. 4

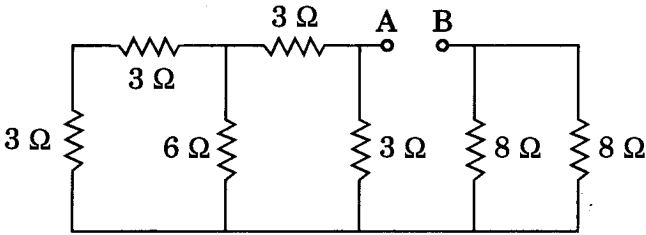


Figure 1

2. (a) A 3-phase balanced load has per phase impedance  $Z_p = (3 + j4)$  ohm and it is star-connected. The supply voltage is 400 volt. Calculate : 6
- (i) Phase voltage
  - (ii) Line current
  - (iii) Power in 3-phase load
- (b) Calculate the maximum power dissipated by resistance R in Figure 2. 8

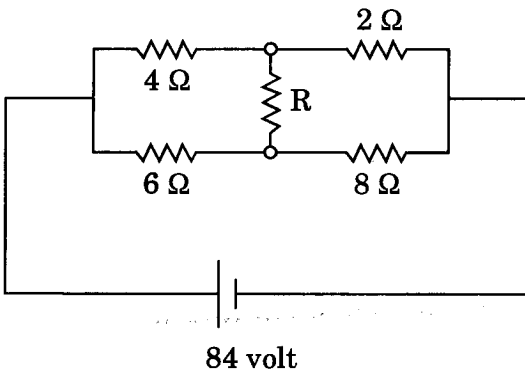


Figure 2

3. Discuss the following :  $4 \times 3 \frac{1}{2} = 14$
- Principle of Transformer Operation
  - Load Characteristics of DC Generators
  - Universal Motor
  - Braking of DC Motors
4. (a) Draw and explain the equivalent circuit of a transformer referred to secondary side. 7
- (b) Explain the Ward-Leonard method for speed control of a DC motor. 7
5. Discuss the following :  $4 \times 3 \frac{1}{2} = 14$
- Regulated DC Power Supply
  - CMOS Inverter
  - Log Amplifier
  - Monostable Multivibrators
6. (a) Design a phase-shift oscillator for a frequency of 10 kHz. 4
- (b) Draw a four-input OR-gate circuit using diode and write its truth table. 6
- (c) Write the applications of CRO. 4
7. Explain the working and applications of the following :  $2 \times 7 = 14$
- Analog-to-Digital Converters
  - 8085 Microprocessor

8. (a) Define Interrupts. Explain various interrupts in 8085 microprocessor. 7
- (b) Design a memory circuit to interface a 4 kbyte RAM to an 8085 microprocessor with starting address  $7000_H$ . 7
-