

**B.Tech. - VIEP - ELECTRICAL ENGINEERING
(BTELVI)**

Term-End Examination

00192

December, 2017

**BIEE-008 : ELECTRO-MECHANICAL ENERGY
CONVERSION - I**

Time : 3 hours

Maximum Marks : 70

Note : *Attempt any **seven** questions out of ten. All questions carry equal marks. Use of scientific calculator is allowed. Make suitable assumptions, if needed.*

1. (a) Develop the phasor diagram of a single-phase transformer under load conditions. Assume lagging power factor load. 5
- (b) Why is the short-circuit test performed on the hv-side of a transformer ? Why is the core loss almost negligible in this test ? 5
2. (a) Explain Sumpner's test for testing two single-phase transformers. 5
- (b) Explain why Sumpner's test is beneficial for finding the efficiency of transformers. 5

3. What are the disadvantages of current and voltage harmonics in transformers ? Explain how these harmonics can be eliminated. 10
4. (a) Discuss briefly the essential and desirable conditions to be fulfilled for operating two three-phase transformers in parallel. 5
- (b) Draw and explain schematically how a three-phase transformer can be connected with another three-phase transformer. 5
5. (a) Describe Swinburne's test with the help of a neat diagram to find out the efficiency of a d.c. machine. 7
- (b) What are the main advantages and disadvantages of this test ? 3
6. (a) Why is the starting current very high in a d.c. motor ? How does the starter reduce the starting current to a safe value ? What are the drawbacks of three-point starter ? 5
- (b) Describe the four-point starter with a neat sketch. 5
7. What is Armature Reaction ? Describe the effects of armature reaction on the operation of d.c. machines. How is the armature reaction minimized ? 10

8. (a) Derive the EMF and torque equation of a d.c. generator. 5
- (b) Neatly sketch and explain the external characteristics of a d.c. compound generator. 5
9. A 120 V d.c. shunt motor having an armature circuit resistance of 0.2Ω and field circuit resistance of 60Ω , draws a line current of 40 A at full load. The brush voltage drop is 3 V and rated full-load speed is 1800 rpm.
- Calculate : 5+5
- (a) The speed at half load
- (b) The speed at 125 percent full load
10. (a) Distinguish between Singly excited and Doubly excited systems. 5
- (b) For a singly-excited linear magnetic system, derive an expression for the electromagnetic torque. 5