

**B.Tech. - VIEP - ELECTRICAL ENGINEERING  
(BTCLVI)**

**00852** Term-End Examination

**December, 2017**

**BIEE-014 : NETWORK THEORY**

*Time : 3 hours*

*Maximum Marks : 70*

---

*Note : Attempt five questions in all. All questions carry equal marks. Assume missing data suitably. Use of scientific calculator is allowed.*

---

---

1. (a) Define the concept of network graph in network graph theory. 2
- (b) Define the following terminologies used in a network graph with appropriate examples : 4×3=12
- (i) Branch
  - (ii) Node
  - (iii) Tree
  - (iv) Loop

2. (a) State and explain the Reciprocity theorem. 7
- (b) State Thevenin's theorem. Derive the expression for Thevenin's resistance ( $R_{th}$ ) and Thevenin's voltage ( $V_{th}$ ) for a two-port network. 7
3. (a) State the Superposition theorem, and prove the theorem. 7
- (b) Find the load impedance in the following figure for maximum power to load. Find the amount of maximum power. 7

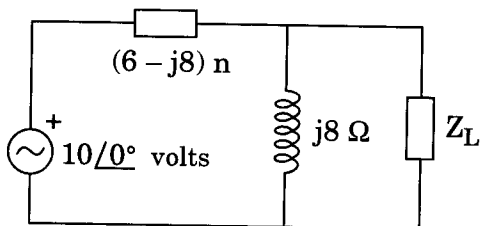


Figure 1

4. (a) What is Network Function ? Give the expressions for different transfer functions of a two-port network. 7
- (b) Discuss the time domain behaviour of transfer function from pole-zero plot. 7
5. (a) Define the following terms :  $2 \times 3 \frac{1}{2} = 7$
- (i) Linear and Non-linear elements
- (ii) Active and Passive elements

(b) For a two-port network, derive the Z-parameters. 7

6. (a) Define the condition of reciprocity and symmetry in two-port parameter representation. 4

(b) For the h-parameter equivalent network (Figure 2), find the voltage gain. 10

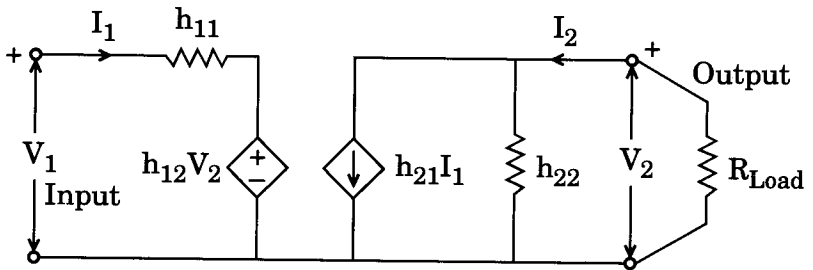


Figure 2

7. Explain in detail, any **two** of the following :  $2 \times 7 = 14$

- (a) Properties of Hurwitz Polynomial
- (b) Analysis of Prototype Low Pass Filter
- (c) Foster and Cauer Forms