

**B.Tech. – VIEP – ELECTRICAL ENGINEERING
(BTELVI)**

00392 Term-End Examination

December, 2017

BIEE-017 : DIGITAL ELECTRONICS

Time : 3 hours

Maximum Marks : 70

Note : *Attempt any seven questions. All questions carry equal marks. Missing data, if any, may be suitably assumed and mentioned. Use of scientific calculator is permitted.*

1. Simplify the following Boolean expressions to a minimum number of literals using laws of Boolean algebra :

$5 \times 2 = 10$

(a) $(x + y)(x + \bar{y})$

(b) $xyz + \bar{x}y + xy\bar{z}$

(c) $xz + \bar{x}yz$

(d) $xy + x(wz + w\bar{z})$

(e) $\bar{a}bc + ab\bar{c} + abc + \bar{a}b\bar{c}$

2. Find the complement of $F = wx + yz$ and also prove that

(a) $F \cdot \overline{F} = 0$,

(b) $F + \overline{F} = 1$. $2+4+4=10$

3. For the given Boolean function :

$$F = \overline{x} \overline{z} + \overline{y} \overline{z} + y\overline{z} + xy, \text{ determine}$$

(a) the function F as a product of maxterms,

(b) Minimal POS expression,

(c) F as a sum of minterms. $3+3+4=10$

4. What is a Full Adder ? Give its truth table. From its truth table, obtain the expression for sum and carry. Also implement a full adder using 2 half adders and an OR gate. $2+2+2+4=10$

5. (a) Implement a 4×16 decoder with the help of 3×8 decoders. 5

(b) Implement the Boolean function
 $F(x, y, z) = \Sigma (1, 2, 6, 7)$ using 4×1 MUX. 5

6. How can a T flip-flop be obtained using

(a) JK flip-flop ?

(b) D flip-flop ? $5+5=10$

7. Explain with the help of a pin diagram, the architecture of 8085 CPU. 10
8. Explain the various addressing modes of 8086. 10
9. Explain the procedure for synthesis of a 3-bit counter using T flip-flop. Support your answer with the state table and logic diagram. 10
10. Write short notes on any *two* of the following : $2 \times 5 = 10$
- (a) Assembler Instruction Format
 - (b) String and Stack Manipulation
 - (c) Comparison of 8088 with 8086
-