

**B.Tech. - VIEP - ELECTRICAL ENGINEERING  
(BTELVI)**

00022

**Term-End Examination**

**December, 2017**

**BIEE-020 : ELECTRICAL MACHINES AND  
ELECTRONICS**

*Time : 3 hours*

*Maximum Marks : 70*

---

**Note :** *Attempt any **seven** questions. All questions carry equal marks. Use of scientific calculator is permitted.*

---

---

1. Deduce the relationship between the phase and line voltages and currents of a three-phase star-connected system. Also draw the phasor diagram. 10
2. Each phase of a three-phase,  $\Delta$ -connected load consists of an impedance  $Z = 20 \angle 60^\circ \Omega$ . The line voltage is 440 V at 50 Hz. Compute the power consumed by each phase impedance and the total power. What will be the readings of the two wattmeters connected ? 10

3. Describe the procedure of conducting open circuit and short circuit tests on a single phase transformer. Derive the expressions of equivalent circuit parameters of core and windings. 10
4. What are the different types of losses in a transformer ? Define efficiency of a transformer and derive the expression for condition of maximum efficiency. 10
5. With the help of proper phasor diagrams, prove that a 3-phase AC source connected to an induction motor produces a rotating magnetic field in the air gap. 10
6. A 150 kW, 3000 V, 50 Hz, 6-pole star-connected induction motor has a star-connected slip ring rotor with a transformation ratio of 3.6. The rotor resistance is 0.1  $\Omega$ /phase and leakage inductance is 3.61 mH/phase. Find the starting current and starting torque on rated voltage with short circuited slip rings. 10
7. What are the advantages of electrical drives ? What are the main factors that decide the choice of electric motor for a drive application ? 10

8. What are the different methods of turning on a thyristor ? Explain any one in detail. 10
9. Write short notes on any **two** of the following : 2×5=10
- (a) Measurement of Reactive Volt-Amperes
  - (b) Welding Transformer
  - (c) Dynamic Characteristics of Electric Drives
  - (d) Operation of a Chopper
-

