

**B.Tech. – VIEP – ELECTRICAL ENGINEERING
(BTELVI)**

Term-End Examination

00902

December, 2017

BIEE-024 : POWER ELECTRONICS

Time : 3 hours

Maximum Marks : 70

***Note :** Attempt any **seven** questions. All questions carry equal marks. Use of scientific calculator is permitted. Assume suitable data, wherever not provided.*

1. Explain the working of Gate Turn-off Thyristors (GTO). Also draw its I – V characteristics. 10
2. It is required to operate a 250-A SCR in parallel with a 350-A SCR with their respective on-state voltage drops of 1.6 V and 1.2 V. Calculate the value of resistance to be inserted in series with each SCR so that they share the total load of 600 A in proportion to their current ratings. 10
3. Describe the gate trigger circuit for a single-phase full converter. Discuss how the adjustment of control voltage varies the firing-delay angle. 10

4. Explain the need of commutation in thyristor circuits. Also, distinguish between voltage commutation and current commutation in thyristor circuits. 10
5. A single-phase full converter delivers power to a resistive load R. For AC source voltage V_s , show that the average output voltage V_o is given by 10
- $$V_o = \frac{\sqrt{2} V_s}{\pi} (1 + \cos \alpha).$$
6. A step-up chopper has input voltage of 220 V and output voltage of 660 V. If the non-conducting time of the thyristor-chopper is 100 μ s, compute the pulse width of output voltage. Also find the new output voltage if pulse width is halved for constant frequency operation. 10
7. Explain sinusoidal pulse-width modulation inverters. Discuss the conditions under which the number of pulses generated per half cycle are $\frac{f_c}{2f}$ or $\left(\frac{f_c}{2f} - 1\right)$, where f_c and f are the frequencies of carrier and reference signals, respectively. 10
8. Describe the basic principle of working of single-phase to single-phase step-down bridge-type cycloconverter for both continuous and discontinuous conductions with the help of neat illustrations. 10

9. Explain the operation of a transistor based 3-phase bridge inverter with resistive load in 120° conduction mode, with the help of suitable circuits and waveforms. 10
10. Write short notes on any *two* of the following : $2 \times 5 = 10$
- (a) MOS Controlled Thyristors
 - (b) Dual Converter
 - (c) Effect of Source Impedance on the Performance of Converters
-