

**B.Tech. MECHANICAL ENGINEERING
(COMPUTER INTEGRATED
MANUFACTURING) /
B.Tech. (AEROSPACE ENGINEERING) (BTAE)**

Term-End Examination

00102

December, 2017

**BME-021 : PRINCIPLES OF ELECTRICAL AND
ELECTRONICS SCIENCE**

Time : 3 hours

Maximum Marks : 70

Note : *Answer seven questions in all. Question no. 1 is compulsory. Answer any three questions from Section A and any three questions from Section B.*

1. State whether the following statements are *True* or *False* : *10×1=10*
- (a) The unit of specific resistance of a conductor is ohm-cm.
 - (b) To reduce eddy current loss in the core of a magnetic material, the core is laminated and the material should have high resistivity.
 - (c) A flip-flop can store more than one bit of information.

- (d) The current in a resonance parallel L-C circuit will be very small.
- (e) The induced e.m.f. in the transformer secondary will depend on the frequency only.
- (f) The condition for maximum torque in an induction motor is $X_2 = SR_2$.
- (g) In p-type semiconductors, the majority carriers are electrons.
- (h) A bridge rectifier is not suitable for low voltage rectification.
- (i) Boolean algebra is essentially based on 2-valued logic.
- (j) 8085 microprocessor has 32-bit address.

SECTION A

Answer any *three* questions from this section.

2. (a) State and explain Thevenin's theorem with suitable example. 5
- (b) Calculate the capacitance and energy stored in a parallel plate capacitor which consists of two metal plates each 60 cm^2 separated by a dielectric of 1.5 mm thickness and $\epsilon_r = 3.5$, if the potential difference of 1000 V is applied across it. 5
3. (a) The inductance of two coils is 25 mH when connected in series and 6 mH when connected in parallel. Calculate the inductance of each coil. 5
- (b) State and explain Kirchhoff's current and voltage laws. 5
4. (a) What do you understand by Real power, Reactive power and Apparent power? 5
- (b) Show that the form factor of the sinusoidal waveform is 1.11 . 5
5. (a) Show that $(E_1/E_2) = (I_2/I_1) = (N_1/N_2)$ in a transformer. 5
- (b) Draw the torque - slip curve of a 3-phase induction motor and mark on it the starting torque, maximum torque and full load torque. 5
6. (a) Compare Intrinsic and Extrinsic semiconductor materials with examples. 5
- (b) Draw and explain the $V - I$ characteristic of a zener diode. 5

SECTION B

Answer any **three** questions from this section.

7. (a) Show how the amplifier is used as (i) an inverting amplifier, and (ii) as a non-inverting amplifier. Give respective gain equations. 5
- (b) Discuss in brief, the operation of SCR. 5
8. (a) Explain the use of 555 timer I.C. as a monostable multivibrator. 5
- (b) Explain the function of tristate inverter and buffer with the help of switches. 5
9. Discuss in detail, the architecture of 8085 microprocessor with diagram. 10
10. (a) What is the difference between volatile and non-volatile memory? 5
- (b) What are Shift Registers? What are the different types of shift registers? 5
11. Write short notes on any **two** of the following : $2 \times 5 = 10$
- (a) Counters
- (b) DeMorgan's Theorem
- (c) 2051 Microcontroller
- (d) TRIAC