

**DIPLOMA IN MECHANICAL ENGINEERING
(DME)**

Term-End Examination

December, 2017

00257

BEE-042 : ELECTRONICS

Time : 2 hours

Maximum Marks : 70

*Note : Question no. 1 is **compulsory**. Answer any **four** questions from the remaining questions.*

1. State *True* or *False* for the given statements : $7 \times 2 = 14$
- (a) A zener diode is operated in the breakdown region.
 - (b) The most commonly used amplifier is the CB connected transistor.
 - (c) P-type materials have holes in minority and free electrons in majority.
 - (d) Seismic type transducer is used to measure velocity.
 - (e) UJT can be used as a relaxation oscillator.
 - (f) ULSI is the most complex of digital ICs.
 - (g) Ripple factor is the ratio of DC voltage to ripple voltage.

2. (a) Draw and explain a Bridge Rectifier with waveform. 7
- (b) Explain the following : 7
- (i) Zener breakdown
- (ii) Avalanche breakdown
3. (a) What is a transistor ? Derive the relation between α_{dc} and β_{dc} . 7
- (b) Explain the following with truth table and logic circuit : 7
- (i) JK Flip-flop
- (ii) RS Flip-flop
4. (a) Describe the principle and application of a CRO with a neat diagram. 7
- (b) With the help of a block diagram, explain each component of a monochrome television transmitter circuit. 7
5. (a) What is an SCR ? Draw and explain the volt - ampere (VI) characteristics of an SCR. 7
- (b) Explain the difference between UJT and FET. Also, draw the symbol of each. 7
6. Write short notes on any *two* of the following : $2 \times 7 = 14$
- (a) Full Adder
- (b) LVDT
- (c) Radio Communication System