

**DIPLOMA - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI) /
ADVANCED LEVEL CERTIFICATE COURSE IN
ELECTRONICS AND COMMUNICATION
ENGINEERING (ACECVI)**

00989

Term-End Examination

December, 2017

BIEL-028 : CIRCUITS AND NETWORKS

Time : 2 hours

Maximum Marks : 70

Note : Attempt five questions in all. Question no. 1 is compulsory. All questions carry equal marks. Symbols used have their usual meaning. Use of scientific calculator is permitted.

1. Choose the correct answer from the given four alternatives :

$$7 \times 2 = 14$$

- (a) In Figure 1, the value of resistance R in ohm is

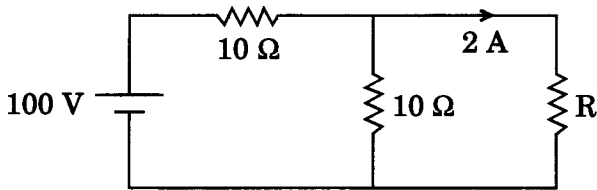


Figure 1

- (i) 10
- (ii) 20
- (iii) 30
- (iv) 40
- (b) A practical current source is represented by
- (i) A resistance in series with an ideal current source
- (ii) A resistance in parallel with an ideal current source
- (iii) A resistance in parallel with an ideal voltage source
- (iv) None of the above

- (c) The current through the $2\text{ k}\Omega$ resistance in the circuit shown in Figure 2 is

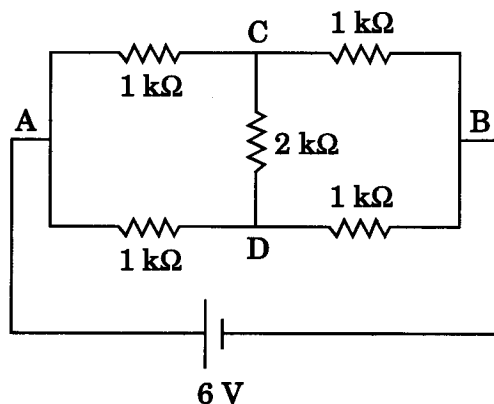


Figure 2

- (i) 0 mA
 (ii) 1 mA
 (iii) 2 mA
 (iv) 6 mA
- (d) The switch in the circuit (Figure 3) has been closed for a long time. It is opened at $t = 0$. At $t = 0^+$, the current through the $1\text{ }\mu\text{F}$ capacitor is

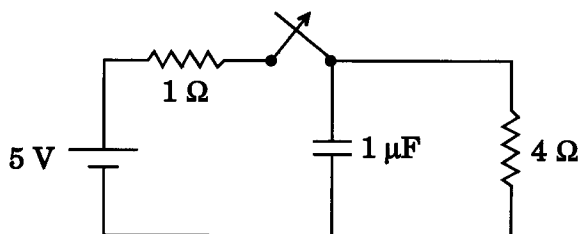


Figure 3

- (i) 0 A
 (ii) 1 A
 (iii) 1.25 A
 (iv) 5 A

- (e) For the two-port network shown in Figure 4, the Z-matrix is given by

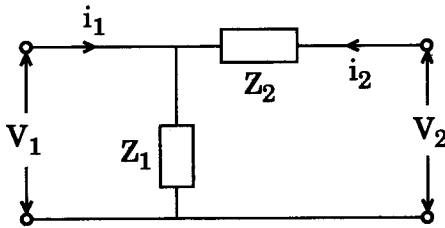


Figure 4

(i)
$$\begin{bmatrix} Z_1 & Z_1 + Z_2 \\ Z_1 + Z_2 & Z_2 \end{bmatrix}$$

(ii)
$$\begin{bmatrix} Z_1 & Z_1 \\ Z_1 + Z_2 & Z_2 \end{bmatrix}$$

(iii)
$$\begin{bmatrix} Z_1 & Z_2 \\ Z_2 & Z_1 + Z_2 \end{bmatrix}$$

(iv)
$$\begin{bmatrix} Z_1 & Z_1 \\ Z_1 & Z_1 + Z_2 \end{bmatrix}$$

- (f) The time constant of the network shown in Figure 5 is

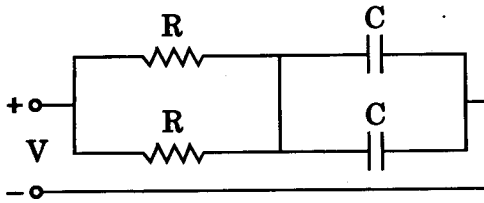


Figure 5

- (i) CR
(ii) 2CR
(iii) CR/4
(iv) CR/2
- (g) In a parallel RL circuit, if I_R is the current in the resistor and I_L is the current in the inductor, then
- (i) I_R lags I_L by 90°
(ii) I_R leads I_L by 270°
(iii) I_L leads I_R by 270°
(iv) I_L lags I_R by 90°

2. (a) State the Superposition theorem with suitable example.

7

- (b) Draw the Thevenin's equivalent of the circuit shown in Figure 6 and find the load current.

7

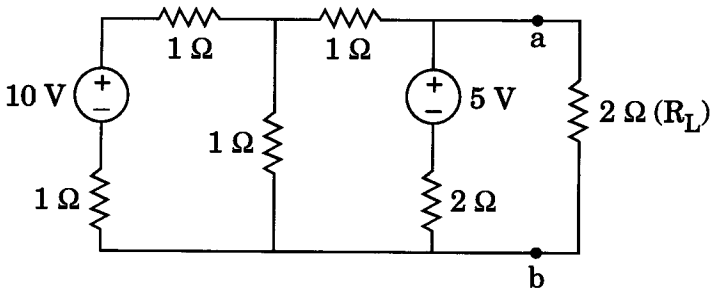


Figure 6

3. (a) A 15 mH inductor is in series with a parallel combination of 80 Ω resistor and 20 μF capacitor. If the angular frequency of the applied voltage is $\omega = 1000$ radians/second, find the admittance of the network.
- (b) A 10 mH coil is connected in series with a loss-free capacitor to a variable frequency source of 20 V. The current in the circuit has a maximum value of 0.2 A at a frequency of 100 kHz. Calculate the
- value of capacitance,
 - Q-factor of the coil, and
 - half power frequencies.

7

7

4. (a) Determine the transmission parameter of the network shown in Figure 7. 7

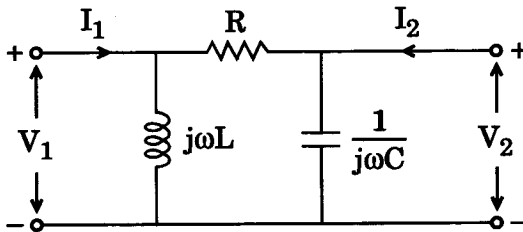


Figure 7

- (b) Define Transfer Function with a suitable example. 7

5. (a) Design a prototype band pass filter having cut-off frequencies of 4 kHz and 6 kHz and a nominal characteristic impedance of 628 Ω . 7

- (b) Calculate the driving point and transfer impedance of the network shown in Figure 8. 7

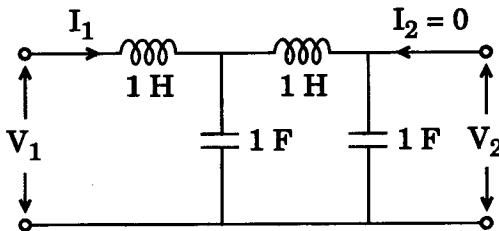


Figure 8

6. (a) Find the initial and final values of the following function, using initial value and final value theorems respectively : 7

$$\frac{s - 1}{(s + 1)(s + 2)}$$

- (b) A coil of resistance 40Ω and inductance 0.75 H forms part of a series circuit for which resonant frequency is 55 Hz . If the supply is 250 V , 50 Hz , find the

- (i) line current,
- (ii) power factor,
- (iii) power consumed, and
- (iv) voltage across the coil. 7

7. Write short notes on any *two* of the following : $2 \times 7 = 14$

- (a) Maximum Power Transfer Theorem
 - (b) Interconnection of Two-Port Networks
 - (c) Hybrid Parameters
-