

**DIPLOMA - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI) /
ADVANCED LEVEL CERTIFICATE COURSE IN
ELECTRONICS AND COMMUNICATION
ENGINEERING (ACECVI)**

Term-End Examination

00919

December, 2017

BIEL-030 : DIGITAL ELECTRONICS

Time : 2 hours

Maximum Marks : 70

Note : Attempt any **five** questions. Question no. 1 is **compulsory**. Use of scientific calculator is allowed.

1. Choose the correct answer for the following : $7 \times 2 = 14$

(a) The NAND gate output will be low if the two inputs are

- (i) 0 0
- (ii) 0 1
- (iii) 1 0
- (iv) 1 1

(b) What is the binary equivalent of the decimal number 368 ?

- (i) 101110000
- (ii) 110110000
- (iii) 111010000
- (iv) 111100000

- (c) The simplification of the Boolean expression $\overline{(\overline{A} \overline{B} \overline{C})} + \overline{(A \overline{B} C)}$ is
- (i) 0
 - (ii) 1
 - (iii) A
 - (iv) BC
- (d) The number of control lines for an 8-to-1 multiplexer is
- (i) 2
 - (ii) 3
 - (iii) 4
 - (iv) 5
- (e) How many flip-flops are required for mod 16 counter ?
- (i) 5
 - (ii) 6
 - (iii) 3
 - (iv) 4
- (f) EPROM contents can be erased by exposing it to
- (i) Ultraviolet rays
 - (ii) Infrared rays
 - (iii) Burst of microwaves
 - (iv) Intense heat radiations

- (g) A ring counter consisting of five flip-flops will have
- (i) 5 states
 - (ii) 10 states
 - (iii) 32 states
 - (iv) Infinite states
2. (a) What is a Flip-Flop ? What is the difference between a latch and a flip-flop ? List out the applications of a flip-flop. 1+3+3=7
- (b) With relevant diagram, explain the working of master slave JK flip-flop. 7
3. Design a BCD to seven-segment decoder that accepts a decimal digit and generates the appropriate output for segments in a display indicator. 14
4. (a) What are the advantages of CMOS logic ? Explain CMOS inverter with the help of a neat circuit diagram. 7
- (b) What is Tri-state logic ? Explain tri-state logic inverter with the help of a circuit diagram. Give its truth table. 7

5. (a) Draw the logic diagram of a full subtractor using half subtractors and explain its working with the help of truth table. 7
- (b) Explain how a shift register can be used as a ring counter giving the waveforms at the output of the flip-flops. 7
6. (a) Reduce the following equation using K-map : 7
$$Y = \overline{A}\overline{B}\overline{C} + A\overline{C}\overline{D} + A\overline{B} + ABC\overline{D} + \overline{A}BC$$
- (b) Write the expression for the Boolean function
 $F(A, B, C) = \sum m(1, 4, 5, 6, 7)$ in standard POS form. 7
7. (a) Distinguish between ROM, PROM, EPROM and EEPROM. 7
- (b) Design a synchronous counter using IC 74191. 7
-