

**B.Tech. – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING (BTECVI)**

Term-End Examination

December, 2017

00989

BIELE-004 : RF CIRCUITS

Time : 3 hours

Maximum Marks : 70

Note : Attempt any **seven** questions. All questions carry equal marks. Missing data may be suitably assumed. Use of scientific calculators is permitted.

1. Explain the characterization of the following IC components at Radio Frequency (RF) : 5+5=10
 - (a) Resistors
 - (b) Inductors

2. Determine the impedance $[Z]$ and the admittance $[Y]$ matrix for a generic pi-network when represented as a two-port network. 5+5=10

3. Describe the classical two-port noise theory with necessary mathematical expressions. 10

4. What are Low Noise Amplifiers (LNA) ? Explain LNA topologies in detail. 3+7=10

5. Explain the large signal performance of an LNA with the help of a neatly labelled diagram. 10
6. What are RF power amplifiers ? Discuss in detail, the operation of a class-B RF power amplifier. $3+7=10$
7. How is the process of modulation carried out in power amplifiers ? Explain with the help of a suitable example. 10
8. What are Oscillators ? Give the criterion for a circuit to act as an oscillator. Explain the various applications of oscillators. $2+3+5=10$
9. Write short notes on any **two** of the following : $2 \times 5 = 10$
- (a) Interconnectors at RF
 - (b) Diode Ring Mixers
 - (c) Noise Model for Resistors
 - (d) Combination Synthesizers
-