

**DIPLOMA IN ELECTRICAL ENGINEERING
(DELVI) / ADVANCED LEVEL CERTIFICATE
COURSE IN ELECTRICAL ENGINEERING
(ACELVI)**

00882

Term-End Examination

December, 2017

**BIEE-030 : INDUSTRIAL DRIVES AND
CONTROLS**

Time : 2 hours

Maximum Marks : 70

Note : *Question no. 1 is compulsory. Attempt any five questions. Use of scientific calculator is permitted.*

1. Attempt the following objective type questions : $7 \times 2 = 14$

(a) The output voltage of a fully controlled converter is maximum when the firing angle is

- (i) zero
- (ii) $\pi/2$
- (iii) 2π
- (iv) $3\pi/2$

- (b) In a three-phase fully controlled converter, the freewheeling diode comes into operation and improves the
- (i) load current
 - (ii) input power factor
 - (iii) Both (i) and (ii)
 - (iv) Neither (i) nor (ii)
- (c) A DC motor can be represented as
- (i) R load
 - (ii) RL load
 - (iii) RLC load
 - (iv) RLE load
- (d) The source inductance of VSI is _____ CSI.
- (i) more than
 - (ii) less than
 - (iii) equal to
 - (iv) half the
- (e) Choppers can be used in
- (i) First quadrant
 - (ii) Second quadrant
 - (iii) Fourth quadrant
 - (iv) All of the above

- (f) The output wave of a chopper is
- (i) non-sinusoidal
 - (ii) sinusoidal
 - (iii) same as input
 - (iv) None of the above
- (g) Closed loop control of drives provide
- (i) Enhancement of speed of response
 - (ii) Protection
 - (iii) Improving accuracy
 - (iv) All of the above

2. A 400 V, three-phase AC supply feeds a separately excited DC motor through two three-phase full converters, one for armature and the other for field. The firing angle of the field converter is zero. The armature current is equal to a rated value of 50 A. The motor voltage constant is 1.3 V/A-rad/sec. The speed is 1200 rpm. Find the firing angle of the converter in the armature circuit. Given $R_a = 0.3 \Omega$ and $R_f = 250 \Omega$. 14

3. Explain the operation of a single-phase fully controlled converter-fed DC separately excited motor. Draw the wave shapes of output voltage and derive its expression. Also show the current wave shape for continuous conduction. 14

4. Derive the speed – torque expression of a DC separately excited motor. Explain the operation of a chopper-fed DC separately excited motor and draw the wave shapes of output voltage. 14
5. What are the methods of speed control of an induction motor ? Explain the variable frequency control of an induction motor by a cycloconverter. 14
6. Draw the complete block diagram for the closed loop control of a DC motor drive. Explain each block and justify how it can improve the accuracy. 14
7. Write short notes on any *two* of the following : $2 \times 7 = 14$
- (a) Closed Loop Control of an Induction Motor Drive
 - (b) Four Quadrant Operation of a Chopper-fed DC Drive
 - (c) Advantages of Continuous Current Operation of a DC Drive
-