

**B.Tech. – VIEP – ELECTRICAL ENGINEERING
(BTELVI)**

Term-End Examination

00319

December, 2017

**BIEEE-013 : POWER QUALITY ISSUES AND
REMEDIAL MEASURES**

Time : 3 hours

Maximum Marks : 70

*Note : Attempt any **seven** questions. Each question carries equal marks. Use of scientific calculator is allowed.*

1. What are the various causes responsible for poor power quality ? Write various power quality standards. 10

2. Define the following basic terminologies related to power quality : $4 \times 2 \frac{1}{2} = 10$
 - (a) Voltage sag and swell
 - (b) Flicker
 - (c) Harmonic content
 - (d) Noise

3. (a) Explain the effects of harmonics on power system equipments. 5
- (b) How does SMPS introduce harmonics into the power system ? Explain with the help of wave shapes. 5
4. Explain the complete monitoring scheme and compensation techniques for mitigating voltage sag. 10
5. Describe the operation of a Static Var Compensator (SVC) with the help of a suitable schematic diagram. 10
6. An induction motor is connected to a 280 V single phase 60 Hz AC source. The real power output of the motor is 350 W at 0.6 p.f. (lagging). Calculate the value of the capacitor to be added, so that p.f. can be improved to unity. 10
7. Discuss the construction and working of a dynamic voltage restorer. 10
8. (a) What are the different grounding problems associated with wiring installations ? 6
- (b) Discuss the solutions for grounding problems in wiring installations. 4

9. Write short notes on any *two* of the following : *2×5=10*

- (a) Shunt Injection Filter
 - (b) Automatic Power Factor Correction (APFC)
 - (c) STATCOM
-