No. of Printed Pages: 4

B.Tech. – VIEP – ELECTRICAL ENGINEERING (BTELVI)

Term-End Examination

December, 2018

00453

BIEE-014 : NETWORK THEORY

Time : 3 hours

Maximum Marks : 70

Note : Attempt any **five** questions. All questions carry equal marks. Use of scientific calculator is allowed.

 (a) Draw the oriented graph of the network shown in Figure 1 and write the incidence matrix.

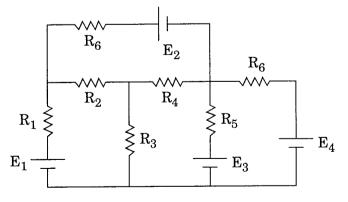


Figure 1

BIEE-014

P.T.O.

- (b) Define the following terms with respect to network topology and give examples : 4
 - (i) Oriented and unoriented graph
 - (ii) Fundamental cut set
- 2. (a) State and explain the maximum power transfer theorem when load impedance is consisting of variable resistance and variable reactance.
 - (b) Determine the Thevenin equivalent circuit which may be used to represent the given network at the terminal A – B.

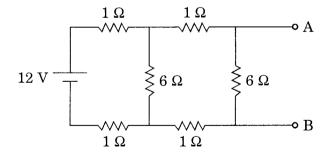


Figure 2

3. (a) Enlist the restrictions on location of poles and zeros in driving point function.

BIEE-014

2

7

(b) Determine the driving point impedance function of the network shown in Figure 3.

7

7

7

7

7

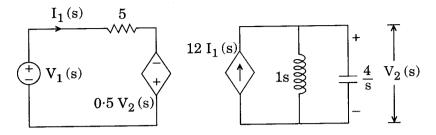


Figure 3

- (a) Obtain the relationship between h and y-parameters of a two-port network.
 - (b) The z-parameters of a two-port network are $z_{11} = 15$ ohms, $z_{22} = 25$ ohms, $z_{12} = z_{21} = 5$ ohms. Determine the ABCD parameters.

- (b) Test whether
 - (i) The polynomial $F(s) = s^4 + 6s^3 + 2s^2 + s + 1$ is Hurwitz or not.
 - (ii) The function $F(s) = \frac{s^3 + 4s^2 + 7s + 3}{s^3 + 3s^2 + 5s + 6}$ is

positive real or not.

BIEE-014

P.T.O.

6. (a) Synthesize the function $z(s) = \frac{4(s+1)(s+3)}{s(s+2)}$ using the Cauer form-I of realization.

(b) Check whether the following functions are of RL, RC or LC types :

(i)
$$\frac{s^3 + 2s}{s^4 + 4s^2 + 3}$$

(ii) $\frac{s^2 + 8s + 15}{s^2 + 3}$

i)
$$\frac{s + 6s + 18}{s^2 + 6s + 8}$$

- 7. Write short notes on any two of the following: $2 \times 7 = 14$
 - (a) Compensation Theorem
 - (b) Advantages and Limitations of Active Filters
 - (c) Properties of Driving Point Function

7