

**B.TECH. IN COMPUTER SCIENCE AND
ENGINEERING (BTCSVI)**

Term-End Examination

June, 2012

BICS-009 : LOGIC DESIGN

Time : 3 hours

Maximum Marks : 70

Note : Attempt any seven questions.

All questions carry equal marks.


1. (a) Implement the given boolean function using only NAND gates 5

$$F = A(CD + B) + B\bar{C}$$
- (b) Simplify and find the minimal SOP and POS circuit for the boolean function : 5

$$F(A, B, C, D) = \sum m(6, 8, 9, 10, 11, 12, 13, 14, 15)$$
2. (a) Simplify the following Boolean function using Quine Mc Clusky method 6

$$f(x_1, x_2, x_3, x_4) = \sum m(0, 5, 7, 8, 9, 10, 11, 14, 15)$$
- (b) Realize $Y = \bar{A}B + \bar{B}\bar{C} + ABC$ using an 8:1 multiplexer. 4
3. (a) Explain programmable Array Logic. 5
- (b) Design a 1 bit binary magnitude comparator. 5

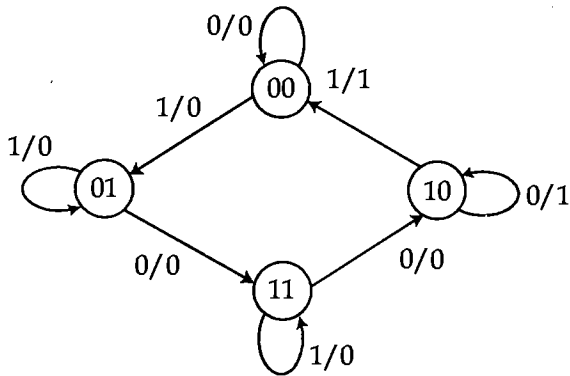4. (a) Add +39 and -22 in 2's complement method. 4
 (b) Design a full adder using two half adders. 6
5. (a) Explain Schmitt Trigger transfer characteristic. 5
 (b) Convert a T - flipflop to D - flipflop. 5
6. (a) For the given state diagram, draw the clocked sequential circuit using T - flipflops. 6



- (b) Explain serial in serial out shift register. 4
7. (a) Design a synchronous 3 bit binary up counter using T - flipflop. 6
 (b) Explain a 4 bit ring counter using D - flipflop. 4

8. (a) What are the problems faced in asynchronous sequential circuits ? 5
- (b) An asynchronous sequential circuit is described by the excitation function : 5
- $$y = x_1\bar{x}_2 + x_1y$$
- and output function
- $$z = x_1x_2y$$
- (i) Draw the logic diagram of circuit.
- (ii) Derive the transition table and output map.
9. Write short notes on *any two* : 10
- (a) A/D converter - counter method
- (b) Dual slope A/D converter
- (c) D/A converter using binary ladder
10. Write short notes on *any two* : 10
- (a) Open collector TTL NAND gate
- (b) 74COO CMOS NAND gate
- (c) MOSFET as a switching circuit.
-