

01145

**B.Tech. IN ELECTRICAL ENGINEERING**

**Term-End Examination**

**June, 2012**

**BIEE-020 : ELECTRICAL MACHINES AND  
ELECTRONICS**

*Time : 3 hours*

*Maximum Marks : 70*


---

*Note : Answer any seven questions in all.*

---

1. Explain how do you measure 3-phase power and Power factor angle with two wattmeters. Draw phasor diagrams. 10
  
2. (a) Draw and explain equivalent circuit of 1- $\phi$  transformer. 5  
(b) A 50 kVA transformer has an efficiency of 98% at full load, 0.8 p.f and an efficiency of 96.9% at  $\frac{1}{4}$  full load, unity p.f. Determine the iron loss and full load copper loss. 5
  
3. (a) Draw the phase diagram of a single phase transformer under loaded condition with lagging power factor. 5  
(b) Derive the condition for maximum efficiency of a transformer. 5

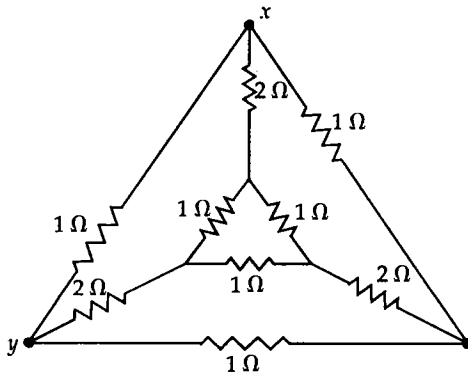4. Explain the production of rotating magnetic field in 3 phase induction motors. 10
5. Explain why single phase induction motor is not self starting and describe the different methods of its starting. 10
6. Draw and explain volt-ampere characteristic and Switching characteristic of an SCR. 10
7. What is a chopper ? Draw and explain a chopper circuit with waveforms. 10
8. Explain in detail the factors affecting selection of motors for industrial use. 10
9. (a) A delta load of  $Z_{AB} = 52 \angle 45^\circ \Omega$  ; 5  
 $Z_{BC} = 52 \angle -30^\circ \Omega$  and  $Z_{CA} = 10 \angle 0^\circ \Omega$  are connected to a 230 V, 3 phase source. Find the magnitude of the line currents, when the phase sequence is ABC.
- (b) Determine the resistance between the point x and y for the network given below. 5



10. Write short note on *any two* of the following :  $2 \times 5 = 10$

- (a) Welding Transformer
  - (b) Slip - Torque characteristic of 3- $\phi$  induction motor
  - (c) Control of dc motors by power electronic devices.
-