

**DIPLOMA IN ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI)/
ADVANCED LEVEL CERTIFICATE COURSE IN
ELECTRONICS AND COMMUNICATION
ENGINEERING (ACECVI)**

Term-End Examination 00400

June, 2012

BIEL-028 : CIRCUITS AND NETWORKS

Time : 2 hours

Maximum Marks : 70

Note : First question is compulsory and Attempt any five questions from 2 to 8, each question carry equal marks.

1. (a) For even function, the necessary condition is: 2x7=14

(i) $f(t) = -f(-t)$

(ii) $f(t) = +f(-1)$

(iii) $f(t) = \frac{1}{f(-t)}$

(iv) $f(t) = -(t \pm T/2)$

(b) The laplace transform of $f(t) = t$ is given by :

(i) $\frac{1}{S^2}$ (ii) $\frac{1}{S}$

(iii) $\frac{2}{S^3}$ (iv) S

(c) A two port network is symmetrical if :


(i) $Z_{11}Z_{22} - Z_{12}Z_{21} = 1$

(ii) $AD - BC = 1$

(iii) $h_{11}h_{12} - h_{12}h_{21} = 1$

(iv) $y_{11}y_{22} - y_{12}y_{21} = 1$

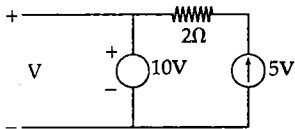(d) The voltage V in the circuit shown in fig. :



(i) 10 V

(ii) 15 V

(iii) 5 V

(iv) None of these

(e) Convolution of $x(t+5)$ with impulse function $\delta(t-7)$ is equal to :

(i) $x(t-12)$

(ii) $x(t+12)$

(iii) $x(t-2)$

(iv) $x(t+2)$

(f) The average value of the half-wave rectified sine wave of amplitude A_m is :

(i) $\frac{A_m}{\pi}$

(ii) $\frac{A_m}{\sqrt{2}}$

(iii) $\frac{A_m}{2}$

(iv) $\frac{2A_m}{\pi}$

(g) In a two-port network containing linear bilateral passive circuit elements, which one of the following condition for Z Parameters would hold :

(i) $Z_{11} = Z_{22}$

(ii) $Z_{12}Z_{21} = Z_{11}Z_{12}$


(iii) $Z_{11}Z_{12} = Z_{22}Z_{21}$

(iv) $Z_{12} = Z_{22}$

2. Attempt *any two* parts :

7x2=14

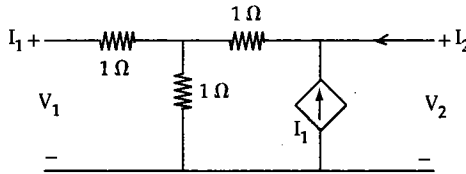- (a) Determine ABCD parameters for the network in fig. :



- (b) Discuss Norton theorem with the help of suitable example.

3. (a) Explain Impedance transformation in resonance circuits. 7x2=14


- (b) Discuss super position theorem with example. How it is helpful in Network analysis.

4. (a) Discuss the significance of pole and zero in Network function. 14


(b) If $F(s) = \frac{s(s+1)}{(s+4)(s^2+4s+Q)}$ find $f(t)$ using 14

the pole-zero diagram of the functions.

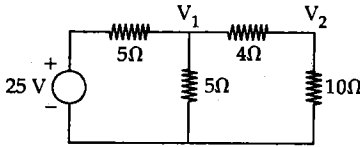5. (a) Determine the voltage across the 10Ω resistor using Nodal analysis in fig. 14




- (b) Determine the current in Branch BD where galvanometer is connected in fig. 14

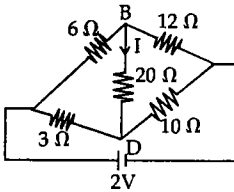


6. Attempt *any two* parts : 7x2=14

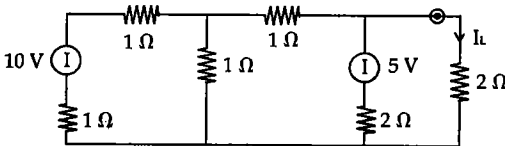- (a) Draw the Thevenin's equivalent of the circuit given in and find the load current in 2Ω resistor fig.




- (b) Discuss the maximum power transfer theorem and prove maximum power will be $P = E^2/4R$.

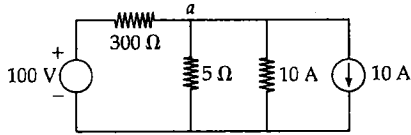- (c) Determine current through 5Ω resistor using Norton theorem in fig.



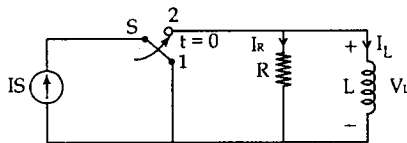7. (a) Determine the current through the Inductor L for $t \geq 0$ as a parallel RL circuit. The switch has been its position 1 for a long time and then moved to position 2 at $t=0$ circuit shown in fig. 14



- (b) Explain the series resonance in the circuit 14
also discuss the fig of merit.
8. Attempt *any two* for writing short notes : 7x2=14
- Hybrid parameters.
 - Constant K-Type Low Pass Filter.
 - T-type Attenuator
 - Interconnection of two port Network.