

00295

**DIPLOMA IN ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI)/
ADVANCED LEVEL CERTIFICATE COURSE IN
ELECTRONICS AND COMMUNICATION
ENGINEERING (ACECVI)**

Term-End Examination

June, 2012

BIEL-030 : Digital Electronics

Time : 2 hours

Maximum Marks : 70

Note : Attempt any five Questions. Question No. 1 is compulsory. Each question carry equal marks.

Attempt all the multiple choice and True/false questions.

1. (a) Which of the following code is the example of self complementry code : **2x7=14**
- (i) Excess - 3 (ii) BCD
(iii) ASCII (iv) Graycode
- (b) Dual of the expression $A.\bar{B}+\bar{C}.D$ is :
- (i) $(\bar{A} B) (C \bar{D})$
(ii) $(A+\bar{B}).(\bar{C}+D)$
(iii) $(A+B) (C+D)$
(iv) None of the above

(c) Expression of sum (S) and carry (C_0) for full adder is :

(i) $S = A \oplus B \oplus C$ $C_0 = AB + BC_{in} + AC_{in}$

(ii) $S = A.B.C$ $C_0 = AB + BC_{in}$

(iii) $S = AB + C$ $C_0 = ABC_{in} + C_{in}B$

(iv) None of these

(d) How many flipflop are required for MOD 6 counter :

(i) > 2 (ii) 3

(iii) 4 (iv) 5

(e) In Moore Model the final output depends only on the present state of memory Element. (T/F)

(f) Adder is an example of sequential circuit. (T/F)

(g) CMOS is slower than TTL (T/F)

2. (a) Prove the following :

7

(i) $A \oplus B = \overline{A} \oplus \overline{B}$

(ii) $B \oplus (B \oplus A.C) = AC$

(b) Convert given base - 7 Number $(35614)_7$ into base 12.

7

3. Minimize following boolean function using K - map and implement logic circuit. 7+7=14

(a) $f(A, B, C, D) = m\{0, 3, 5, 6, 9, 10, 12, 15\}$
Using NOR gate

(b) $f(A, B, C, D) = m\{0, 1, 5, 7, 9, 14, 15\} + d\{2, 6, 8\}$ using NAND gate only.

4. What is multiplexer ? What are the application of multiplexer ? Draw 16 : 1 multiplexer using 4 : 1 multiplexer. 14
5. Draw the logic diagram of the following flipflops. Also construct the excitation table, characteristic equation of each. 14
- (a) Clocked SR flipflop, JK flipflop, T flipflop
- (b) D flipflop and master slave flipflop.
6. For the state diagram shown in Fig 1. obtain the state table and design the circuit using minimum number of T flip flop. 14

 


Fig. 1

7. (a) What is meant by open collector output of TTL gate ? What is its utility ? Draw and explain the open collector output and pull up register. 7
- (b) Draw and Explain CMOS, NOR and NAND gate diagram. 7

8. Write short note on any four of the following :

3.5x4=14

- (a) All 4 bit shift registers
 - (b) Steps to design decade asynchronous counter.
 - (c) Expansion of Memory
 - (d) Full adder and full subtractor.
 - (e) D/A converter and A/D converter
 - (f) Difference between Moore and Mealy M/Cs.
-