

DIPLOMA IN ENGINEERING

Term-End Examination

June, 2012

BIELE-006 : ELECTRONIC PRODUCT DESIGN

Time : 2 hours

Maximum Marks : 70

Note : 1. Attempt *any five* questions.

2. Question No. 1 is *compulsory*.

1. (a) What do you mean by regulated Power supply ? **2x7=14**
(b) How to detect over current in a circuit/system ?
(c) Explain the working of MCB.
(d) Name any two simulation software for design of circuits.
(e) What is Bandstop filter ? How it can be obtained ?
(f) State the working principle of A-D converter.
(g) What is Relay and state its use ?

2. Design a FSM for sequence detector that produces 1 if it detects 1001 or 010 in the incoming data bit sequence. Draw the circuit using D flip-flops. **14**

3. What is ASM technique ? Describe various steps involved in traffic light controller design. **14**

4. For the circuit of Fig 1 show that :

14

$$\frac{V_2}{V_1} = \frac{-(G_1/C_1)s}{s^2 + s(G_1 + G_2)/C_2 + G_1G_2/C_1C_2}$$

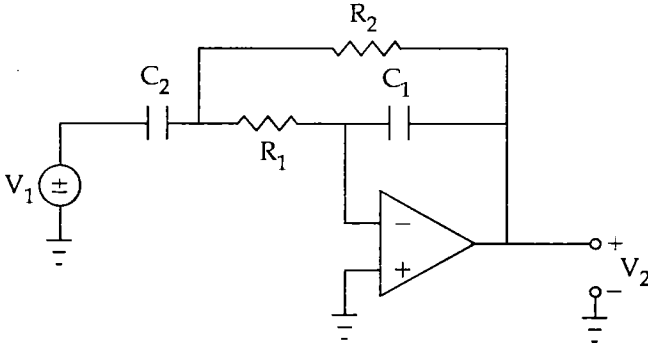


Fig. 1

5. What is KRC filter ? Give KRC realization for low pass filter and obtain expressions for filter parameters. Find component values for following specifications. 14

$f_0 = 4.8 \text{ KHz}$, $Q = 5$ and gain = 2.8

6. Discuss the basic characteristics and conditioning requirements of some common transducers. Discuss briefly any two transducers. 14

7. Explain interfacing of relay with microcontroller. Give complete schematic and instructions. 14

8. Write short note on *any four* of the following :

- (a) Mealy and Moore machines **3¹/₂x4=14**
 - (b) Logic implementation with PAL
 - (c) Higher order filter design
 - (d) DAC interfacing
 - (e) Thermal considerations
 - (f) Indicators for over voltage
-