

**DIPLOMA IN ELECTRICAL ENGINEERING
(DELVI)/ADVANCED LEVEL CERTIFICATE
COURSE IN ELECTRICAL ENGINEERING
(ACELVI)**

Term-End Examination 02969

June, 2012

**BIEE-030 : INDUSTRIAL DRIVES AND
CONTROLS**

Time : 2 Hours

Maximum Marks : 70

-
- Note : (i) All the questions are to be answered in English only.
(ii) Attempt **any five** questions . Question No. 1 is **compulsory**.*
-
-

Attempt the following objective type questions.

1. (a) Fully controlled converter means : 2
- (i) In which a.c. input current is bidirectional.
 - (ii) In which power flow can be in either direction.
 - (iii) In which a.c. input current is unidirectional.
 - (iv) None of the above.
- (b) SCR can be turned ON by applying. 2
- (i) large anode voltage
 - (ii) anode voltage at a fast rate
 - (iii) large gate current
 - (iv) sufficiently large temperature to SCR
 - (v) all of the above

- (c) Which motor should not run on no load or light load ? 2
- (i) D.C . series motor
(ii) D.C. shunt motor
(iii) Induction motor
(iv) D.C. compound motor.
- (d) In a 3-phase , six pulse diode rectifier, the average out put voltage in terms of maximum value of line voltage V_m is 2
- (i) $\frac{3\sqrt{2}V_m}{\pi}$ (ii) $\frac{3V_m}{\pi}$
- (iii) $\frac{3\sqrt{3}V_m}{2\pi}$ (iv) $\frac{3\sqrt{3}V_m}{\pi}$
- (e) In dc choppers, if T_{on} is the on, period and f is the chopping frequency, the output voltage in terms of input voltage V_s is given by: 2
- (i) $\frac{V_s \cdot T_{on}}{f}$ (ii) $\frac{V_s \cdot f}{T_{on}}$
- (iii) $\frac{V_s}{f \cdot T_{on}}$ (iv) $V_s \cdot f \cdot T_{on}$
- (f) In PWM method of controlling the average output voltage in a chopper, the on-time is _____(varied/kept constant) but the chopping frequency is (varied/kept constant) _____ . 2

- (g) Which of the following statement / statements is/are correct in connection with inverters. 2
- (i) VSI & CSI both require feedback diodes
 - (ii) Only CSI requires feedback diodes
 - (iii) GTOs can be used in CSI
 - (iv) Only VSI requires feedback diodes
2. (a) Describe the working of a single phase full converter fed d.c. drive with appropriate voltage and current wave forms. 7
- (b) A 200V, 875 rpm , 150A separately excited dc motor has an armature resistance of 0.06 Ω . It is fed from a single phase fully controlled rectifier with an ac source voltage of 220V, 50Hz. Assuming continuous conduction, calculate 7
- (i) Firing angle for rated motor torque and 750 rpm
 - (ii) Firing angle for rated motor torque and -500 rpm.
3. (a) Give the concept of electric drives. Illustrate your answer with examples. 7
- (b) What is an ac - dc converter ? Explain the working of single phase half wave controlled rectifier using R and R-L load. 7

4. (a) Describe the use of a 3-phase semiconverter for the speed control of a dc series motor. Illustrate your answer with appropriate wave forms. 7
- (b) Derive expressions for the rms values and average values of output current and voltage for 3 -phase semiconverter. 7
5. (a) Distinguish between two quadrant and four quadrant drives. 7
- (b) Describe how a four quadrant drive can be obtained from a chopper fed separately excited dc motor. 7
6. (a) Describe the speed control method of D.C. series motor using chopper. 7
- (b) For step up chopper input voltage is 220V and output voltage is 660V. If the non-conducting time of thyristor chopper is 100NS. Compute the pulse width of output voltage. 7
- In case pulse width is halved for constant frequency operation. Find the new output voltage.
7. (a) What are ac. drives ? Give their merits and demerits with respect to dc drives. 7
- (b) Induction motor speed control with constant supply voltage and reduced supply frequency is rarely used in practice, justify the statement. 7

8. Write short notes on *any four* : 3½x4=14

- (a) Closed loop operation of D.C. drives
 - (b) Three phase full converter drives
 - (c) Comparison of VSI and CSI
 - (d) Speed control of D.C .drives
 - (e) Slip torque characteristic of induction motor drive
 - (f) Step up chopper.
-