

**B.Tech. Civil (Construction Management) /
B.Tech. Civil (Water Resources Engineering)**

Term-End Examination

June, 2013

**ET-202(B) : PRINCIPLES OF ELECTRICAL
SCIENCES**

Time : 3 hours

Maximum Marks : 70

Note : Attempt any five questions in all. Use of calculator is permissible.

1. (a) Explain working principle of a transformer and calculate the r.m.s value of induced emf in the secondary winding of a transformer when a sinusoidal flux 0.2 Wb(max) links with 55 turns of a transformer secondary winding. 6
- (b) What do you understand by 'armature reaction' ? What is the effect of armature reaction in a d.c. generator ? 6
- (c) Mention the relative advantages and disadvantages of using a digital indicating instrument over an analog instrument. 2

2. (a) Give relationship between line and phase quantities (voltage and current) in a star connected circuit and show them on a phasor diagram. 6

- (b) A capacitor draws a current of 5 mA from 200V, 50 Hz a.c supply. What current does it draw from 40V , 400 Hz supply. 6
- (c) A balanced three phase load is formed by three impedances of $60 + j90$ ohms each, connected in delta. If this load is equivalent to a star connected load having \bar{Z}_y in each leg of the star, calculate \bar{Z}_y . 2
3. (a) What are the basic components used in electrical installations ? State briefly the functions of each component. 6
- (b) Explain the necessity of power factor correction. What are different methods for power factor correction ? 6
- (c) What is instrument transformer ? Write its features. 2
4. (a) Draw and explain speed-torque characteristics of a d.c series motor. 6
- (b) A d.c machine generates an armature voltage of 220V on no load at 1000 rpm , the field current being 2A. The armature resistance is 0.5Ω . Find its speed when it draws a current of 5A as motor from the 220V supply. (Neglect armature reaction and brush voltage drop). 6
- (c) A Lissajous pattern obtained on a CRO screen has $f_y = 50$ Hz. Number of touching points on horizontal tangent = 5 and number of touching points on a vertical tangent = 3. Find f_x . 2

5. (a) A 3- phase induction motor is wound for 4 poles and is supplied from a 50Hz system. Calculate : 6
- (i) Actual speed of the motor when running at 4% slip.
- (ii) Frequency of emf induced in the motor.
- (b) Explain briefly the various methods of controlling speed of DC shunt motor. 6
- (c) For any two terminal network draw Thevenin equivalent circuit. 2
6. (a) Explain how diodes operate as AC to DC converter with the help of circuit diagrams. 6
- (b) What is the basic principle of CRO ? Explain its two applications. 6
- (c) Draw characteristics of an ideal operational amplifier. 2
7. (a) Explain the working of a dual slope integrating type ADC. 6
- (b) What are different addressing modes available in 8085 microprocessor ? Give an example of each mode. 6
- (c) Find the decimal equivalent of : 2
- (i) $(1110101)_2$
- (ii) $(101011)_2$
-