

**B. TECH
BTCSVI / BTECVI / BTELVI**

Term-End Examination

June, 2013

**BIEL-001 : BASICS OF ELECTRONICS
ENGINEERING**

Time : 3 Hours

Maximum Marks : 70

Note : (i) *Attempt any seven questions.*

(ii) *Assume missing data if any.*

(iii) *Use of scientific calculator is permitted.*

1. (a) With the help of energy band diagram, explain why some materials behave as insulators, some as good conductors and others as semiconductors. 5
- (b) Define : 5
- (i) Mean life time of a carrier
- (ii) Diffusion length
2. What is Zener effect ? Explain the function of a Zener diode and draw its characteristics. 10

3. (a) How does a tunnel diode differ from a conventional P-N junction diode ? 5
- (b) Determine the current flowing in the circuit shown in fig. (i). Also determine the potential of point A. 5

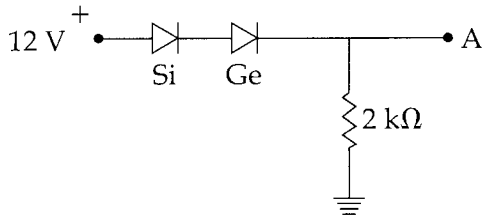


Fig. (i)

4. For the common emitter circuit of fig. (ii), calculate the values of I_B , I_C , I_E and V_{CE} . Take $\beta = 50$ and neglect V_{BE} . 10

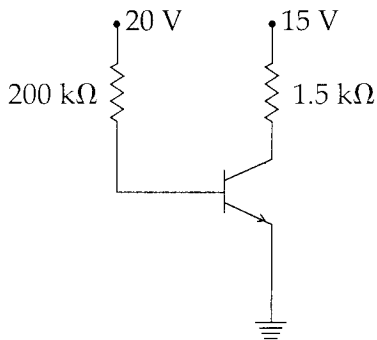


Fig. (ii)

5. With neat sketch, describe the construction and working of UJT. Define the term "Intrinsic stand-off ratio". 10
6. (a) Describe the basic principles of photo transistors. 5
(b) Draw the equivalent circuit of UJT and explain all parameters. 5
7. Describe briefly the construction and operation of a MOSFET in depletion region. 10
8. (a) What do you mean by ripple factor and peak inverse voltage ? 5
(b) What is Bleeder resistance ? Why it is used in L-C filter ? 5
9. Draw the circuit diagram and explain the working of full wave rectifier using semi-conductor diodes. 10
10. Write short notes on *any two* : 2x5=10
(a) Varactor diode
(b) Voltage multipliers
(c) LDR
-