

**B.TECH. ELECTRONICS AND  
COMMUNICATION ENGINEERING  
(BTECVI)**

**Term-End Examination**

**June, 2013**

**BIEL-003 : DIGITAL ELECTRONICS**

*Time : 3 hours*

*Maximum Marks : 70*

---

*Note : Attempt seven questions in all. All the questions to be answered in English-language only.*

---

- |    |     |  |   |
|----|-----|--|---|
| 1. | (a) | Subtract using $r$ 's complement<br>$(0.1101)_2 - (111.01)_2$  | 5 |
|    | (b) | Convert the BCD number (011110010001)<br>to its decimal equivalent.  | 5 |
| 2. | (a) | Proof of De-Morgan's theorem using Truth table.  | 5 |
|    | (b) | Simplify using k-map the given function.<br>$F(A, B, C, D) = \pi M(0, 3, 5, 11, 13, 14, 15)$<br>$+ d(7, 8, 9, 12)$ | 5 |
| 3. | (a) | Design 4 bit Gray to Binary code converter using 1:16 demultiplexer (with active low output).                      | 5 |
|    | (b) | Design 4:16 line decoder using 3:8 decoders.   | 5 |

4. (a) Realise the function using 16:1 MUX 5  
 $f(w, x, y, z) = \sum m(0, 3, 4, 7, 9, 13, 15)$
- (b) Combinational circuit is defined by the 5  
function  
 $F_1(A, B, C) = \sum (3, 5, 6, 7)$   
 $F_2(A, B, C) = \sum (0, 2, 4, 7)$   
implement the circuit with PLA.
5. (a) Draw ASM chart for 2-bit down counter 5  
having one enable input  $x$ , count is enabled if  $x=0$  and disable if  $x=1$ .
- (b) Design a MOD-5 counter of states (0, 3, 4, 5  
6, 7). Ensure that all unused states reset to zero automatically.
6. (a) Draw the logic diagram of D flip-flop and 5  
write characteristic table.
- (b) Draw the logic diagram of T flip-flop and 5  
write excitation table.
7. (a) Construct  $16 \times 8$  RAM memory using  $16 \times 4$  5  
RAM memory ICs.
- (b) Design a BCD to Excess-3 code converter 5  
using PLA.
8. (a) Design MOD-10/ Decode/BCD 5  
synchronous counter using J - K flip flop.
- (b) What happens if any input of TTL circuit is 5  
kept floating ?

9. (a) Design a BCD to seven segment decoder using PROM. 5
- (b) Design a BCD to seven segment decoder using PLA. 5
10. (a) Write a short note on Gray Code. 5
- (b) Write a short note on Excess-3 Code. 5
-