

**B.Tech. ELECTRONICS AND  
COMMUNICATION ENGINEERING (BTECVI)**

**Term-End Examination**

**June, 2013**

**BIEL-005 : ANALOG ELECTRONIC CIRCUITS**

*Time : 3 hours*

*Maximum Marks : 70*

- 
- Note :** (i) Attempt *any five* questions.  
(ii) All questions carry *equal* marks.  
(iii) All the questions are to be answered in English language only.  
(iv) Use of scientific calculator is *permitted*.
- 

1. (a) What are the h-parameters of a linear circuit ? Define them. 7
- (b) A CE amplifier has the following h - parameters : 7
- $$h_{ie} = 1100 \text{ ohm} \quad h_{re} = 2.5 \times 10^{-4}$$
- $$h_{fe} = 50 \quad h_{oe} = 25 \text{ micromho}$$
- if load and source resistance both are 1 kilo - ohm, find current gain and voltage gain.
2. (a) What are the various methods of cascading a two stage transistor amplifier ? Discuss their relative advantages and disadvantages. 7

- (b) The gain of an amplifier is 50 its collector resistance  $R_C = 600\Omega$  and the input impedance  $R_{in} = 1.2k\Omega$ . Calculate overall gain when two such amplifier are cascaded through R-C coupling. Comment on the results. 7
3. (a) Draw the hybrid  $\pi$ -model of BJT in CE connection and derive equation for current gain. 7
- (b) A BJT has  $g_m = 38$  m mho,  $r_{b'e} = 5.9k\Omega$ ,  $h_{ie} = 6$  k $\Omega$ ,  $r_{bb'} = 100\Omega$ ,  $C_{b'e} = 63$ PF and  $h_{fe} = 224$  at 1KHz. Calculate  $\alpha$  and  $\beta$  cut-off frequencies and  $f_T$  gain-band width product. 7
4. (a) Define class A, B and C amplifiers, giving their relative merits and demerits. 7
- (b) Draw the circuit diagram of push-pull amplifier and explain its working. 7
5. (a) Draw the circuit diagram of double-tuned amplifier. Explain how the frequency response of this amplifier is better than that of single-tuned amplifier ? 7
- (b) Draw the series resonant circuit. Plot a curve showing the variations of circuit current with frequency, and explain it briefly. 7

6. (a) Distinguish current feedback and voltage feedback with appropriate circuit diagram. 7
- (b) Draw the circuit diagram of emitter follower and explain its working. 7
7. (a) Draw the circuit diagram of R - C phase shift oscillator and explain its working. 7
- (b) With neat sketch explain briefly the operation of Colpitts Oscillator. 7
8. Write short notes on **any two** : 7x2=14
- (a) Monostable multi-vibrator
- (b) 555 Timer
- (c) UJT
-