

00085

**B.TECH. - VIEP-ELECTRICAL ENGINEERING**

**Term-End Examination**

**June, 2013**

**BIEE-014 : NETWORK THEORY**

Time : 3 hours

Maximum Marks : 70

- Note :** (i) Attempt *any five* questions.  
 (ii) All questions carry *equal* marks.

1. (a) Find current  $I_N$  for the network shown in fig - 1 using graph theory. 7

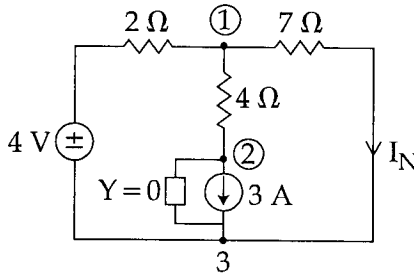


Fig. 1

- (b) Draw the dual of the network as shown in fig - 2. 7

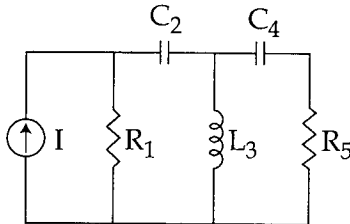


Fig. 2

2. (a) Determine current in the capacitor branch by using super position theorem in the circuit shown in fig - 3. 7

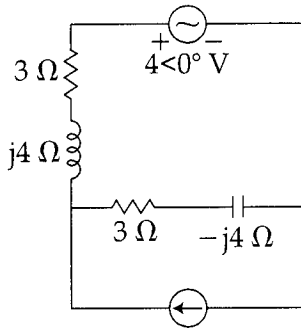


Fig. 3

- (b) State and prove Tellegen's Theorem. 7

3. (a) Find transfer impedance function 7

$Z_{21}(s) = \frac{V_2(s)}{I_1(s)}$  of the network shown in fig - 4.

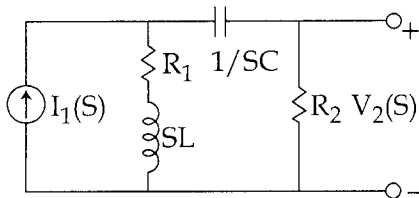


Fig. 4

- (b) Explain various properties and necessary conditions for transfer functions. 7

4. (a) Derive the condition for reciprocity and symmetry in case of T - parameters. 7

- (b) Show that when two networks  $N_1$  and  $N_2$  are connected in parallel, the equivalent Y - parameters of combined network is the sum of Y parameters of each individual 2 port network. 7
5. (a) Test whether following function is a positive real function or not. 7
- $$F(s) = \frac{S^3 + S^3 + 3S + S}{S^2 + 6S + 8}.$$
- (b) Synthesise the given impedance function in Cauer - I form 7
- $$Z(s) = \frac{S(S+2)(S+5)}{(S+1)(S+4)}.$$
6. (a) Design a Low pass filter having a cut - off frequency of 1kHz to operate with a terminated load resistance of 200  $\Omega$ . 7
- (b) What are the limitations of passive filters? 7  
Enlist some of the advantages of active filters.
7. Write short notes on **any three** of following : 5, 5, 4
- Reciprocity Theorem
  - Routh Hurwitz stability criterion
  - Image parameters and characteristics impedance
  - Positive real functions
  - Constant K Type High pass filter.