

01668

**B.TECH. - ELECTRICAL ENGINEERING**

**Term-End Examination**

**June, 2013**

**BIEE-017 : DIGITAL ELECTRONICS**

*Time : 3 hours*

*Maximum Marks : 70*

---

**Note :** *Attempt any seven questions as the following. Assume the missing data if any.*

---

1. Derive the Boolean expression for a two-input Ex-OR gate to realize with two input NAND gates without using complemented variables and draw the circuit. 10
  
2. Express the Boolean function  $F = AB + \overline{A}C$  in a product of maxterm form. 10
  
3. Reduce the expression  $f = \sum m(0, 2, 3, 4, 5, 6)$  using k-map and implement it in NAND logic. 10
  
4. What is full subtractor? Design a full - subtractor and discuss with an example. 10

5. Using a  $4 \times 1$  MUX implement the logic function 10  
 $F(A, B, C) = \sum m(1, 2, 4, 7)$ .
6. What are the sequential circuits and how they are 10  
different from combinational circuits ?
7. What is a master - slave flip-flop and why they 10  
are called pulse - triggered flip-flops ?
8. Explain the internal Architecture of 8085 with the 10  
help of neat diagram.
9. Discuss the Bus-Architecture of 8086 and explain 10  
how 20 bit Address bus is used to address different  
memory segments.
10. Write the short notes on *any two* of the 5x2=10  
following :
- (a) PLA
  - (b) Decoder
  - (c) Shift Registers
-