

00845

B.Tech. ELECTRICAL ENGINEERING

Term-End Examination

June, 2013

**BIEE-020 : ELECTRICAL MACHINES AND
ELECTRONICS**

Time : 3 hours

Maximum Marks : 70

Note : Attempt any five questions in all.

1. (a) Derive the numerical relationship between line and phase currents for a balanced 3 - phase delta connected load. **10**
- (b) State the advantages of A.C. poly phase supply system over a single - phase system. **4**
2. Describe the method of calculating the regulation and efficiency of a single phase transformer by open circuit and short circuit tests. **14**
3. (a) A 200 kVA transformer has an efficiency of 98% at full load. If the maximum efficiency occurs at three quarters of full load, calculate the efficiency at half load. Assume negligible magnetising current and p.f. of 0.8 at all loads. **10**
- (b) Write a short note on welding transformer. **4**

4. (a) Derive an expression for the torque of an induction motor and obtain condition for maximum torque. 10
- (b) A-3 phase, 4 pole, 50 Hz induction motor is running at 1440 rpm. Determine the slip speed and slip. 4
5. (a) Explain the steady state and dynamic characteristics of electric drives. 10
- (b) Name the different parameter on which size of motor depends. 4
6. (a) What is a inverter ? Draw and explain an inverter circuit with waveform. 10
- (b) Why single phase induction motor is not self started ? 4
7. Write short notes on following : 2x7=14
- (a) Load equalization
- (b) Measurement of reactive volt amperes
-