

**DIPLOMA IN ELECTRICAL AND
MECHANICAL ENGINEERING**

Term-End Examination

June, 2013

0 1 3 9 2

BEE - 042 : ELECTRONICS

Time : 2 hours

Maximum Marks : 70

-
- Note :**
- (i) Question No. 1 is *compulsory*.
 - (ii) Attempt *any four* questions of the remaining questions numbered 2 to 8.
 - (iii) Use of calculator is *permitted*.
 - (iv) Each question carries *equal* marks.
-

1. (a) State True or false for the given statements : 7x1=7
- (i) Peak inverse voltage of half wave rectifier is given by $2V_m$.
 - (ii) Output impedance of emitter follower is very high.
 - (iii) The transistor acts as an switch in cut - off and saturation region.
 - (iv) Fan out of TTL logic is 40.
 - (v) Universal logic gates are NAND and NOR.
 - (vi) Bourdon tube is a device which used to measure the specific gravity.
 - (vii) Television has 626 scanning lines.

(b) Select the correct answer from the given four alternatives : 7x1=7

- (i) Transformer utilization factor of full wave rectifier is _____.
- (A) 0.287
 - (B) 0.693
 - (C) 0.21
 - (D) 0.89
- (ii) The outermost electrons of an atom are called _____ electrons.
- (A) valence
 - (B) conduction
 - (C) free
 - (D) bound
- (iii) BJT acts as an amplifier in _____ region.
- (A) active region
 - (B) saturation region
 - (C) cutoff region
 - (D) none of these
- (iv) MSI means _____ .
- (A) less than 12 basic gates per chip
 - (B) 100 - 999
 - (C) 12 - 100 gates per chip
 - (D) 1000-9999 gates per chip

- (v) CRT is also know as :
- (A) willium tube
 - (B) electron tube
 - (C) crookes tube
 - (D) none of the above
- (vi) To obtain Lissajous figure two sinusoidal voltages of equal frequency are applied :
- (A) horizontal and vertical
 - (B) vertical
 - (C) horizontal
 - (D) none of the above
- (vii) AND gate gives output 'high' when :
- (A) both input low
 - (B) both input high
 - (C) one input low and one input high
 - (D) none of the above

2. (a) An ac supply of 230 volt is applied to the primary of a transformer. The transformer has turn ratio of 10 : 1. neglect the diode resistance and transformer resistance. Calculate : 7
- (i) V_{dc}
 - (ii) PIV in a bridge rectifier
- (b) Explain V-I characteristics of zener diode and how zener diode can be used as voltage regulator. 7

3. (a) Compare CB, CE, and CC configurations of BJT. 7
- (b) Explain the functioning of a transistor as an amplifier with a circuit diagram. 7
4. (a) Explain the working of SCR and sketch typical SCR forward and reverse characteristic. 7
- (b) What is scanning in TV ? How it is done ? 7
5. (a) Convert the following : 7
- (i) $(111100)_2 = (?)_{10}$
- (ii) $(19)_{10} = (?)_2$
- (iii) $(B7A)_{16} = (?)_{10}$
- (iv) $(2570)_{10} = (?)_{16}$
- (v) $(317)_{10} = (?)_8$
- (vi) $(28.30)_{10} = (?)_2$
- (vii) $(3A)_{16} = (?)_8$
- (b) Realize a full subtractor using two half subtractor and write the truth table. 7
6. (a) What is principle on which thermo couple works ? List their advantages and disadvantages. 7
- (b) Draw the schematic diagram of LVDT and explain briefly its characteristics. 7

7. (a) With the help of neat sketch explain the working of CRO. What are the application of a CRO ? 7
- (b) With the help of block diagram explain the construction and working of digital frequency meter. 7
8. Write short notes on *any four* of the following ?
- (a) Doping in semiconductor $4 \times 3\frac{1}{2} = 14$
- (b) Biasing of Transistor
- (c) Universal gates
- (d) UJT as a relaxation oscillator
- (e) RVDT
- (f) Advantage of bridge rectifier
- (g) Generalised measuring system
-