

**DIPLOMA VIEP ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI)/
ADVANCED LEVEL CERTIFICATE COURSE IN
ELECTRONICS AND COMMUNICATION
ENGINEERING (ACECVI)**

Term-End Examination

June, 2013

BIEL-030 : DIGITAL ELECTRONICS

Time : 2 hours

Maximum Marks : 70

- Note :** (i) Attempt **any five** questions. Each question carries equal marks.
- (ii) Question no **one** is compulsory (objectives).
- (iii) All the questions are to be answered in English Language only

1. Attempt all objective questions.

- (a) A 4-bit binary number whose 2'S compliment is also same is : $7 \times 2 = 14$
- (i) 0 0 0 1 (ii) 0 1 0 1
- (iii) 0 1 1 1 (iv) 1 0 0 0
- (b) $A + \bar{A} = \underline{\hspace{2cm}}$.
- (i) 0 (ii) 1 (iii) A (iv) \bar{A}
- (c) A demultiplexer is represented by :
- (i) $2^n \times 1$ (ii) $2^n \times n$
- (iii) $n \times 2^n$ (iv) 1×2^n


- (d) Which has the highest power dissipation Per gate.
- (i) TTL
 - (ii) CMOS
 - (iii) ECL
 - (iv) PMOS
- (e) In a left shift register, shifting a bit by one means :
- (i) division by 2
 - (ii) Multiplication by 2
 - (iii) Subtraction of 2
 - (iv) Addition of 2
- (f) A XOR gate has inputs A and B and output Y. Then the output equation is :
- (i) $Y = A\bar{B} + AB$
 - (ii) $Y = AB + \bar{A}B$
 - (iii) $Y = \bar{A}\bar{B} + AB$
 - (iv) $\bar{A}B + A\bar{B}$
- (g) Which is known as Flash converter.
- (i) Weighted resistor D/A converter
 - (ii) Parallel A/D converter
 - (iii) Stair step A/B converter
 - (iv) Up-down counter type A/D converter.

2. (a) Give the binary, BCD, excess - 3, gray code, Hexadecimal and octal representations of decimal numbers 5, and 8. 2x7=14
- (b) Design a binary to gray converter circuit of 3 - bit (variable) ?

3. (a) Simplify the given boolean Function using k-map and implement the minimized expression using Logic gates. $2 \times 7 = 14$

$$f(A, B, C, D) = \sum m(1, 2, 9, 10, 11, 14, 15)$$
- (b) Using NAND gate implement OR, AND, XOR and XNOR gates.
4. (a) Implement 8:1 Multiplexer using 4:1 Multiplexer and explain its operation. $2 \times 7 = 14$
- (b) Design and implement MOD-5 synchronous counter using J - K Flip Flop.
5. (a) With a neat diagram explain the operation of 4 - bit PISO (Parallel Input Serial Output) shift register. $2 \times 7 = 14$
- (b) Draw the truth table of two input NAND gate and NOR gate and implement them using CMOS Logic.
6. (a) Explain the operation of a Master slave J - K flip Flop and show how the race around condition is eliminated. $2 \times 7 = 14$
- (b) Differentiate between SRAM and DRAM.
7. (a) Convert the following functions to canonical Form : $2 \times 7 = 14$
- (i) $y = A + BC + ABC$
- (ii) $y = (A + B) (\bar{B} + C)$

 - (b) Obtain the reduced state table and reduced state diagram for a sequential circuit whose state diagram is shown in figure.



8. Write short notes on **any four**. 3.5x4=14
- Propagation delay and fan in and Fan out.
 - EPROM and EEPROM
 - ECL Logic family
 - BCD Arithmetic
 - Excitation table of Flip Flops.
 - Boolean Algebra - Basic - Laws
