

DECVI

Term-End Examination

June, 2013

BIEL-038 : LINEAR INTEGRATED CIRCUITS

Time : 2 hours

Maximum Marks : 70

-
- Note :** 1. First question is *compulsory* and attempt *any four* from the rest.
2. Use of scientific calculator is *permitted*.
-

1. (a) The maximum values of $+V_{cc}$ and $-V_{cc}$ that can be given to op - amp are _____ . 2
- (b) A common - mode rejection ratio in dB can be expressed as : 2
- (i) $20 \log_{10} \frac{A_{cm}}{A_{dm}}$
- (ii) $20 \log_{10} \frac{A_{cm}}{2}$
- (iii) $10 \log_{10} \frac{A_{dm}}{A_{cm}}$
- (iv) $20 \log_{10} \frac{A_{dm}}{2}$

- (c) A good op - amp has : 2
- (i) very high bandwidth
 - (ii) narrow bandwidth
 - (iii) high selectivity
 - (iv) all of the above.
- (d) An op-amp circuit can function as a comparator if the feedback resistor is made equal to _____ . 2
- (e) The other name of schmitt trigger is : 2
- (i) regenerative comparator
 - (ii) square wave generator
 - (iii) backlash circuit
 - (iv) all of the above
- (f) IC-555 can be used as : 2
- (i) monostable multivibrator
 - (ii) pulse detector
 - (iii) ramp generator
 - (iv) all of the above
- (g) Select correct statement of PLL : 2
- (i) capture range smaller than lock range
 - (ii) lock range smaller than capture range.
 - (iii) capture range is equal to lock range
 - (iv) none of the above.
2. (a) Explain the meaning of bias, offsets, and drift as applied to OP-AMPs. 6
- (b) Sketch an OP-AMP Inverter and explain the circuit operation with relevant waveforms. 8

3. (a) Describe the operation of basic comparator, with relevant waveforms. 6
- (b) Sketch the schematic diagram of a monostable multivibrator and give the expression for the oscillation frequency. 8
4. Draw the circuit diagram of a second order Butterworth high pass filter and explain the principle of operation. 14
5. (a) Explain the operation of PLL. 7
- (b) Design a monostable multivibrator for the output pulse width of 10 ms. 7
6. (a) Draw the set - up for a voltage to current converter, for a grounded load. Mention briefly its operation. 7
- (b) Bring out the important features of a multiplier IC. 7
7. (a) For the three input summing amplifier, derive the expression for the output voltage interms of the inputs and circuit components. 7
- (b) Draw and explain the block diagram of IC-555 Timer. 7

8. Write short notes on *any four* of the following :

(a) Slew rate of OP - AMP

3.5x4=14

(b) Notch filter

(c) Importance of OP - AMP

(d) Sample and Hold circuit

(e) Practical Differentiator

(f) FM demodulator
