

**B.TECH. IN ELECTRONICS AND
COMMUNICATION ENGINEERING (BTECVI)**

Term-End Examination

June, 2013

BIELE-011 : DIGITAL SYSTEM DESIGN

Time : 3 hours

Maximum Marks : 70

*Note : Attempt **any five** questions. All questions carry equal marks.*

1. (a) With a neat block diagram and functional tables, explain the operation of serial adder with accumulator. 10
- (b) What is Digital Design concept ? 4

2. (a) Differentiate between PAL and PLAs. Implement following functions, using a suitable PLA : 10

$$F_1(A, B, C, D) = \sum m(2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$$

$$F_2(A, B, C, D) = \sum m(2, 3, 5, 6, 7, 10, 11, 14, 15)$$

$$F_3(A, B, C, D) = \sum m(6, 7, 8, 9, 13, 14, 15)$$
- (b) Give applications of ROM and PROM. 4

3. (a) Write a VHDL program for the function $Y = AB + C\bar{D}$ using 10
 (i) Behavioral modelling
 (ii) Structural modelling
 (b) What do you mean by Event and Transaction ? Give suitable example. 4
4. (a) Design a 3 digit BCD to binary converter. Draw the block diagram and the state diagram. 10
 (b) Design a 2 bit \times 2 bit multiplier using address and gates. 4
5. (a) Using MSI Decoder design a LST circuits. 10
 (b) Write application of 8×02 in system control design. 4
6. (a) Explain operator overloading with examples. 10
 (b) Draw hazards excitation map by MEV method. 4
7. Write short notes on *any four* of the following :
 (a) Fundamental of sequential machine $3\frac{1}{2} \times 4 = 14$
 (b) Signal attributes
 (c) Signal assignments
 (d) FDLA
 (e) DFD
-