

00300

**B.Tech. ELECTRICAL ENGINEERING
(BTELVI)**

Term-End Examination

June, 2013

**BIEEE-008 : FLEXIBLE AC TRANSMISSION
SYSTEM**

Time : 3 hours

Maximum Marks : 70

Note : *Attempt any seven questions. Each question carry equal marks. Assume suitable missing data, if any.*

1. What is series capacitor compensation ? What are the relative advantages and disadvantages ? Analytically compare between the series and shunt compensation of Transmission line. **10**

2. (a) What do you mean by FACTS ? What are usual FACTS devices ? **5**
(b) What is the difference between FACTS device with and without energy storage ? **5**

3. Why SVC is treated as a shunt controlled FACTS device ? Briefly describe the operation of a SVC. **10**

4. Describe the power flow model of STATCOM. Why does it act as a shunt controller in FACTS Technology ? **10**

5. What is UPFC ? Why it is superior to other conventional FACTS devices ? How would you model UPFC for a power flow program ? 10
6. A delta connected TCR (Thyristor Controlled Reactor) is connected to a 400 kV Transmission line through a 10:1 step-down-transformer. The max reactive power at rated voltage is 100 MVAR. What would be the value of the fundamental component of line-current of TCR at 400 kV side for conduction angle of 120° ? What is the peak current in the thyristor ? 10
7. Explain the basic principle of P and Q power flow control mechanism. 10
8. Write short note on **any two** of the following : $2 \times 5 = 10$
 - (a) TCVR
 - (b) TCPAR
 - (c) Thyristor controlled braking resistor.
9. Briefly describe the interline power flow controller. 10
10. Discuss the advantages of the dynamic compensation at the middle of the Transmission line. 10