

01394

**B.Tech. IN ELECTRICAL ENGINEERING
(BTELVI)****Term-End Examination****June, 2013****BIEEE-016 : INDUSTRIAL DRIVES***Time : 3 hours**Maximum Marks : 70*

Note : (i) Answer *any five* questions.
(ii) Each question carry *equal* marks.

1. (a) State essential parts of electric drives with block diagram. What are the functions of a power modulator ? 7
- (b) What are the different components of load torque ? Draw their characteristics and write the governing equations. 7
2. A 200V, 875rpm, 150A separately excited dc motor has an armature resistance of 0.06Ω . It is fed from a single phase fully controlled rectifier with an ac source of 220V, 50Hz. For continuous conduction, calculate. 14
- (a) firing angle for rated torque and 750rpm
- (b) motor speed for $\alpha = 160^\circ$ and rated torque.

3. (a) What are the different types of braking used in DC motor drives ? Explain regenerative braking with its characteristics. 7
- (b) What are constant torque and constant power control of dc drive ? 7
4. (a) Explain the operation of VSI fed induction motor drive. 7
- (b) Explain the construction and working of a static Scherbius Drive. 7
5. (a) Explain, how rotor resistance control can be used to vary the speed of induction motor without any change in maximum torque. 7
- (b) Describe any method of speed control of single phase induction motor. 7
6. (a) How a self- controlled synchronous motor drive employing a cyclo-converter works ? 7
- (b) Explain the operation of a unipolar brushless dc motor. 7
7. Write short notes on *any two* of the following :
- (a) Phase locked loop speed control 2x7=14
- (b) Solar powered electrical vehicle
- (c) PWM drives
- (d) Chopper fed dc drives
-