

**B.Tech. ELECTRICAL ENGINEERING
(BTELVI)****Term-End Examination****June, 2013****BIEEE-018 : ADVANCED POWER ELECTRONICS***Time : 3 hours**Maximum Marks : 70*

Note : Attempt *seven* questions out of *eight* questions. Each question carries *equal* marks.

1. (a) Describe the switching characteristics of power MOSFETs and compare power MOSFETs with BJTs. 6
- (b) A bipolar transistor having β in range 8 to 40. The load resistance $R_C = 11\Omega$, dc supply voltage $V_{CC} = 200V$, $V_B = 10V$. If $V_{CE}(\text{sat}) = 1.0V$ and $V_{BE}(\text{sat}) = 1.5V$. Find : 4
 - (i) the value of R_B that results in saturation with an overdrive factor 5
 - (ii) Forced β_f
 - (iii) Power loss P_T
2. Explain the working of 3 ϕ full converter with the help of waveforms. Consider the load is resistive. Also derive an expression for average value of o/p voltage. 10

3. (a) Draw the circuit diagram of 3 ϕ square wave inverter and explain its working with the help of waveforms. 6
- (b) What is the effect of blanking time on voltage in PWM inverters ? 4
4. (a) Compare VSI and CSI. What are applications of CSI ? Explain the operation of 1 ϕ capacitor commutated CSI with R load. 7
- (b) Calculate the output frequency of a series inverter with following parameters $L=6$ mH, $C=1.2\mu\text{F}$, load resistance $R=100\ \Omega$ $T_{\text{off}}=0.2$ ms. If load resistance is varied from 40 to 140 ohms, find out the range of o/p frequency. 3
5. (a) Explain the three phase 180 mode of conduction in bridge inverter. Draw the waveforms also. 6
- (b) A three phase bridge inverter is fed from a dc source of 200 V. If the load is star connected of $10\ \Omega$ / phase pure resistance, determine the r.m.s load current, the required r.m.s current rating of thyristor and load power for :
- (i) 120° firing
- (ii) 180° firing

6. Explain the operation of STATCOM and compare it with static var compensator. 10
7. Derive a general expression for the fundamental and harmonic content of a quasi square wave o/p inverter. Plot curves showing harmonic variation against width variation of the wave on period. 10
8. Write short notes on : 10
- (a) GTO
 - (b) IGBT
 - (c) Active power filter
 - (d) Harmonic elimination method
-