

00710

B.Sc. (NAUTICAL SCIENCE)**Term-End Examination****June, 2014****BNA-013 : ELECTRICITY AND ELECTRONICS***Time : 2 hours**Maximum Marks : 70*

-
- Note :** (i) *Non-programmable scientific calculator is allowed.*
(ii) *Attempt three questions from each section.*
(iii) *Questions No. 1 and 5 are compulsory.*
-

SECTION - A
(Electricity)

1. (a) Explain with neat sketch principle, construction and working of AC generator. 10
(b) A 2000/200 V, 20 kVA transformer has 66 turns in the secondary. Calculate the primary turns and primary and secondary full load currents, neglecting losses. 5
2. (a) State and explain Faraday's laws of electromagnetic Induction. 5
(b) A solenoid of length 50 cm is uniformly wound with 500 turns of wire. If a current of 2 A is flowing in it, what is the flux density at its centre ? If the cross-sectional area of the solenoid is 4 cm², what is the total magnetic flux set-up at its centre ? 5

3. (a) Explain R-L-C series circuit in AC circuit. 5
 (b) A moving coil meter has a resistance of 2 ohm and gives full scale deflection with 20 mA. Show how it can be used to measure voltage up to 250 V. 5
4. (a) State and explain ohm's law and its limitations. 5
 (b) An air cored solenoid has 300 turns its length is 25 cm and its cross section is 3 cm^2 . Calculate the self inductance in henry. 5

SECTION - B

(Electronics)

5. (a) Explain the term demodulation with necessary circuit diagram. What are essentials in demodulation ? 10
 (b) The antenna current of an AM transmitter is 8 A when only carrier is sent but it increases to 8.93 A when the carrier is sinusoidally modulated. Find the percentage modulation. 5
6. (a) Explain the operation of transistor as an oscillator. 5
 (b) For a single stage transistor amplifier, the collector load is $R_C = 2 \text{ k}\Omega$ and the input resistance $R_i = 1 \text{ k}\Omega$. If the current gain is 50, calculate the voltage gain of the amplifier. 5

7. (a) Draw the circuit of a practical single stage transistor amplifier. Explain the function of each component. 5
- (b) An amplifier, when loaded by $2\text{ k}\Omega$ resistor, has a voltage gain of 80 and a current gain of 120. Determine the necessary signal voltage and current to give an output voltage of 1 V. What is the power gain of the amplifier? 5
8. Write short notes on any two of the following :
- (a) A. M. Radio Receivers 2x5=10
- (b) Light Emitting Diode (LED)
- (c) Piezo-Electric Crystal
-