

**B.Tech. ELECTRONICS AND  
COMMUNICATION ENGINEERING  
(BTECVI)**

00324

**Term-End Examination**

**June, 2014**

**BIEL-003 : DIGITAL ELECTRONICS**

*Time : 3 hours*

*Maximum Marks : 70*

---

**Note :** *Attempt any seven questions. Each question carries equal marks.*

---

1. (a) What do you mean by a Unit distance code ? Write any such 4-bit code. 3
- (b) Given that  $16_{10} = 100_b$ , find the value of b. 3
- (c) State and prove DeMorgan's theorem. 4
2. Design a circuit that will output a HIGH (1) whenever the 4-bit hexadecimal input is an odd number. Implement the circuit by using NAND gates only. 10
3. (a) Design a Half-subtractor circuit. 5
- (b) What is the disadvantage of serial adders ? For which applications are they preferred ? 5

4. How does a JK flip-flop differ from an S-R flip-flop in its basic operation ? With neat diagram explain the working of a Master-Slave JK flip-flop. 10
  5. Implement a 4-bit synchronous up-down counter using JK flip-flops. Explain its working. 10
  6. What is PROM ? Describe various methods which can be used to erase a PROM. Can a PROM be used to implement a truth table ? Justify your answer. 10
  7. Compare the following technologies : 10
    - (a) TTL and MOS
    - (b) MOS and CMOS
  8. With the help of neat circuit diagrams, explain the working of a two-input standard ECL circuit. 10
  9. (a) How does a static RAM cell differ from a dynamic RAM cell ? Give the circuit diagram for a cell in each. 5
    - (b) What do you mean by Pulse train generator ? State its use. 5
  10. Write short notes on any *two* of the following :  $2 \times 5 = 10$ 
    - (a) ALU
    - (b) Priority encoder
    - (c) PLA
-