

**B.Tech. ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

**00024 Term-End Examination
June, 2014**

BIEL-005 : ANALOG ELECTRONIC CIRCUITS

Time : 3 hours

Maximum Marks : 70

*Note : Attempt any **seven** questions. Assume suitable missing data, if any. Use of scientific calculator is permitted.*

1. Define the h-parameters for a transistor in CB and CE configuration and also discuss these briefly. 10

2. Draw the circuit diagram of an R-C coupled amplifier employing potential divider bias and explain the function of each component. 10

3. A BJT is found to have $f_T = 500$ MHz, $h_{fe} = 100$, $r_{bb'}$ = 100 Ω , $r_{b'e}$ = 900 Ω and $C_{b'c}$ = 5 pF. It is used as a CE amplifier with $R_S = 1$ k Ω and $R_L = 500$ Ω . Determine the amplifier mid-band voltage gain $A_{VS} = \frac{V_0}{V_S}$. 10

4. Draw the circuit of a Class B push-pull amplifier and explain its operation. What is cross-over distortion ? How is it minimised ? 10
5. Discuss briefly the double turned amplifier with a help of its circuit diagram. 10
6. A single stage amplifier has a voltage gain of 10 and a bandwidth of 1 MHz. Three such stages are cascaded and a negative feedback of 10% is applied to the cascade stage. Find the overall voltage gain and bandwidth of the cascaded stage with feedback. 10
7. (a) An oscillator circuit has an inductor of 80 mH and capacitor of 6 pF. Determine the frequency of oscillation. 4
 - (b) Why are R-C oscillators preferred in audio frequency range ? 6
8. With the help of circuit diagram explain the working of monostable multivibrator circuit. Give its waveforms. 10
9. (a) Calculate the frequency of oscillation for an astable multivibrator with $R_1 = R_2 = 1 \text{ k}\Omega$, $C_1 = C_2 = 1 \text{ }\mu\text{F}$. 5
 - (b) State the advantages and disadvantages of tuned amplifiers. 5
10. Write short notes on any *two* of the following : $2 \times 5 = 10$
 - (a) Monostable multivibrator
 - (b) UJT
 - (c) Wein Bridge oscillator