

**B.Tech. – VIEP – ELECTRICAL ENGINEERING
(BTELVI)**

Term-End Examination

00507

June, 2014

BIEEE-012 : ACTIVE FILTER DESIGN

Time : 3 hours

Maximum Marks : 70

***Note :** Attempt any **seven** questions. All questions carry equal marks. Use of calculator is permitted. Missing data may be suitably assumed.*

1. Give the second order s-domain equation for all five types of filter. Also give their pole-zero plot. 10
2. Realize the following specification with a maximally flat magnitude response : 10

$$\alpha_{\max} = 0.5 \text{ dB}, \quad \alpha_{\min} = 20 \text{ dB}$$

$$\omega_p = 1000 \text{ rad/sec}, \quad \omega_s = 2000 \text{ rad/s.}$$

3. For the circuit shown in figure 1, find the transfer function $V_o(s)/V_i(s)$. Identify the response and determine filter parameters. Assume ideal op-amp. 10

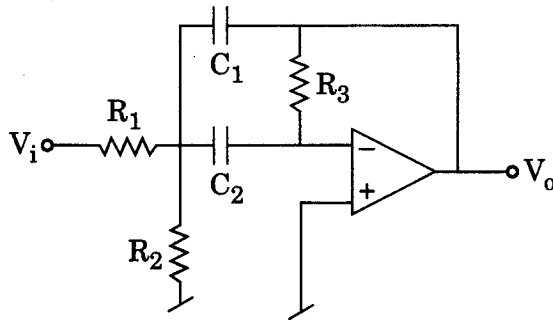


Figure 1

4. Design a Sallen-Key low pass filter with following specifications : 10

$$f_c = 4.8 \text{ kHz}, Q = 5 \text{ and dc gain } H = 3.$$

5. Give the circuit diagram of a KHN filter, obtain the transfer function and identify filter parameters. 10

6. Draw the circuit diagram of a Generalized Impedance Converter (GIC) as given by Antoniou and show how a grounded inductor can be simulated using the above circuit. 10

7. Determine the input impedance (Z_{in}) for the circuit shown in figure 2. Also draw the passive equivalent of the circuit. 10

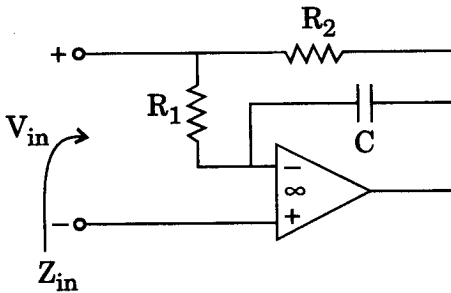


Figure 2

8. Determine the transfer function V_2/V_1 for the circuit shown in figure 3 considering non-ideal op-amp with $A = \omega t/s$. Identify the nature of filter response and determine the filter parameters. 10

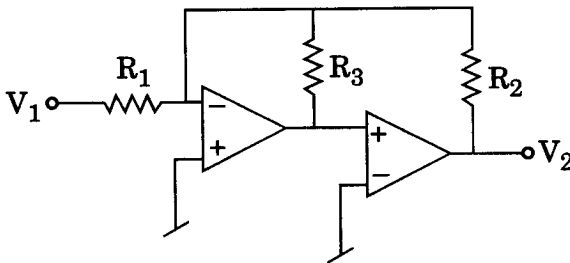


Figure 3

9. Explain the procedure for obtaining higher-order filter (e.g. a fifth order) by cascading of lower-order filters. 10

10. Write short notes on any *two* of the following : $2 \times 5 = 10$

- (i) Butterworth Approximation
 - (ii) Phase-error compensation
 - (iii) Delay-Equalizer functions
-