

**B.Tech. MECHANICAL ENGINEERING  
(COMPUTER INTEGRATED MANUFACTURING) /  
B.Tech. AEROSPACE ENGINEERING (BTAE)**

**Term-End Examination**

01190

**June, 2014**

**BME-021 : PRINCIPLES OF ELECTRICAL AND  
ELECTRONICS SCIENCES**

*Time : 3 hours*

*Maximum Marks : 70*

---

*Note : Answer **seven** questions in all. Question number 1 is **compulsory**. Attempt any three questions from Section A and any three questions from Section B. Use of scientific calculator is permitted.*

---

---

1. State whether the following assertions are true or false :  $10 \times 1 = 10$
- (i) Conductor having high conductivity has high resistivity.
  - (ii) A constant voltage source has zero internal resistance.
  - (iii) Resistance of insulators increases with increase in temperature.

- (iv) Kirchhoff's current law states that the vector sum of the currents meeting at a junction is zero.
- (v) Reluctance is the property of a magnetic material that aids the passage of magnetic flux in it.
- (vi) Piezo-electric effect is one in which an emf is produced when symmetrical crystalline materials are placed under stress.
- (vii) A program counter points to the memory address from which the next machine code is to be collected.
- (viii) An ideal OP-AMP possesses zero gain, zero input impedance and infinite output impedance.
- (ix) ROM (Read Only Memory) is a non-volatile memory.
- (x) A thyristor has low on-state voltage and an even smaller turn-on current.

## SECTION A

Answer any **three** questions from this section.

2. (a) State and explain Norton's theorem. 5
- (b) Find the current through the  $2\ \Omega$  resistance in the network shown in Figure 1 using Thevenin's theorem. 5

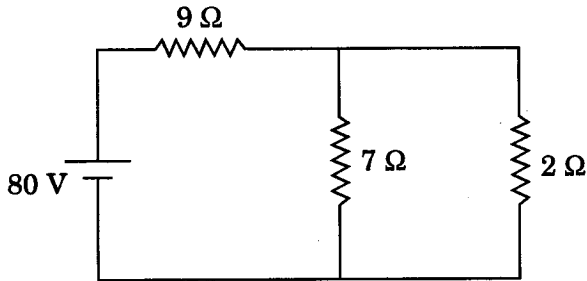


Figure 1

3. (a) Define cycle, time period, frequency, amplitude, phase and phase difference with reference to an a.c. waveform. 6
- (b) A capacitor of  $100\ \mu\text{F}$  is connected in series with a coil of resistance  $5\ \Omega$  and inductance  $0.12\ \text{H}$ . This combination is supplied by a  $500\ \text{V}$ ,  $50\ \text{Hz}$  supply. Calculate
- (i) the rms value of the circuit current
  - (ii) the power factor
  - (iii) the voltage across the capacitor. 4

4. (a) Explain magnetic hysteresis. 5
- (b) A circular ring of mild steel has a diameter of 20 cm and a 2 mm side air gap. The cross-sectional area of the ring is  $3.2 \text{ cm}^2$ . Estimate the mmf required to establish a flux of 0.6 mWb. Assume relative permeability of mild steel equal to 900. 5
5. (a) Compare star and delta connected systems. 5
- (b) Three similar coils each of resistance  $28 \Omega$  and inductance 0.1 H are connected in star. If the supply voltage is 230 V, 50 Hz, calculate the line current and the total power absorbed. 5
6. (a) Explain open circuit (O.C.) and short circuit (S.C.) tests on a transformer. What information do we get from these tests? 6
- (b) Write a brief note on operation of a universal motor. 4

## SECTION B

Attempt any **three** questions from this section.

7. (a) Explain how an ADC (analog to digital converter) works. 5
- (b) Discuss the logical instructions used in a microprocessor with examples. 5
8. (a) Explain the I – V characteristics of a zener diode. 5
- (b) Describe the operation of a full wave bridge rectifier. 5
9. (a) Discuss the blocking operation of an IGBT. 5
- (b) What are the functions of counters ? What is the difference between synchronous and asynchronous counters ? 5
10. (a) State and explain De-Morgan's theorems. Hence verify that  $A + BC = (A + B)(A + C)$ . 7
- (b) Explain the 'AND' and 'OR' logic gates with truth table. 3
11. (a) Explain the use of 555 timer I.C. as a monostable multivibrator. 5
- (b) Discuss the working of SISO (serial in serial out) and SIPO (serial in parallel out) shift registers. 5