

DECVI / DELVI / DCSVI / ACECVI / ACELVI /
ACSVI

00297

Term-End Examination

June, 2014

BIEL-027 : APPLIED ELECTRONICS

Time : 2 hours

Maximum Marks : 70

Note : All questions are to be answered in English Language only. Attempt any five questions including question no. 1 which is compulsory. Use of scientific calculator is permitted.

1. (a) The output of power amplifiers is several times its input power. It is possible because

2

- (i) Power amplifier introduces a negative resistance
- (ii) There is a positive feedback in circuit
- (iii) Step-up transformer is used in circuit
- (iv) Power amplifier converts a part of input D.C. power into A.C. power

(b) A Class B push-pull power amplifier has an A.C. output of 10 Watts. The D.C. power drawn from power supply under ideal condition is

2

- (i) 10 W
- (ii) 12.75 W
- (iii) 15 W
- (iv) 20 W

(c) In amplifier applications, FET is operated

2

- (i) In the controlled resistor region
- (ii) In controlled source region
- (iii) In the avalanche region
- (iv) In none of these

(d) State whether the following statements are *true* (T) or *false* (F) :


2

- (i) Feedback always increases the gain of an amplifier.
- (ii) The closed loop gain of an amplifier is always greater than open-loop gain.

- (e) The Barkhausen criterion gives 2
- (i) Condition for stability
 - (ii) The maximum gain for which there are no oscillations
 - (iii) The phase-shift required for oscillations
 - (iv) The maximum feedback for a stable amplifier
- (f) Clamper circuits are known as 2
- (i) AC restorers
 - (ii) DC restorers
 - (iii) Voltage to frequency converters
 - (iv) Sweep circuits
- (g) For a Miller timebase circuit, the main requirement to obtain the highest linearity is that the amplifier gain should ideally be 2
- (i) $+ 1$
 - (ii) $- 1$
 - (iii) $- \infty$
 - (iv) $+ \infty$
2. (a) Draw the circuit diagram of a complementary symmetry push-pull Class B power amplifier and explain its principle of operation. Also give its advantages and disadvantages. 8

- (b) For Class A, CE amplifier shown in figure below, $(V_{ce})_{\theta} = 10 \text{ V}$, $(I_c)_{\theta} = 500 \text{ mA}$. If the output current varies by $\pm 250 \text{ mA}$ when an input signal is applied at the base, calculate maximum efficiency and overall efficiency.

6

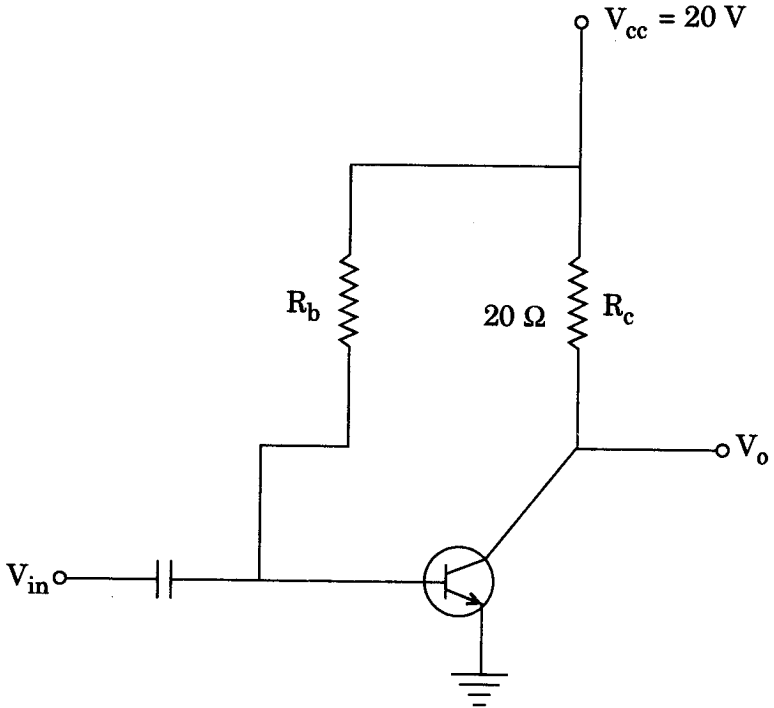

3. (a) With the help of circuit diagram, explain the working of FET as voltage variable resistor (VVR) and give its applications.
- (b) Explain basic construction of an enhancement type N-channel MOSFET. Draw and explain its static characteristics. How is the threshold voltage of MOS-transistor adjusted?

6

8

4. (a) Explain with a circuit diagram the operation of a single-tuned amplifier. Draw its AC equivalent circuit and find the expressions for voltage, gain and bandwidth. 7
- (b) Explain the concept of feedback in amplifiers. What do you mean by positive and negative feedback? 7
5. (a) Draw the circuit diagram of Colpitt's oscillator and explain its operation. What is the approximate frequency of oscillations? 7
- (b) What do you mean by clippers? Draw and mention various kinds of clippers and explain any one. 7
6. (a) Explain with block diagram the working of bistable multivibrator. 7
- (b) Describe the switching characteristics of a transistor. A rectangular pulse of voltage is applied to the base of a transistor. Explain various times that are involved in switching process. 7
7. (a) Draw the circuit diagram of UJT relaxation oscillator and explain its working. 7
- (b) Explain the need for troubleshooting. Which approximations does the technician normally use when performing initial troubleshooting procedures and why? 7

8. Write short notes on any *four* :

$$3\frac{1}{2} \times 4 = 14$$

- (i) Features of time base signals
- (ii) Frequency stability of oscillators
- (iii) Power Amplifiers
- (iv) Clippers and Clampers
- (v) Applications of Schmitt trigger
- (vi) Troubleshooting and Testing