

**DIPLOMA - VIEP - ELECTRONICS AND  
COMMUNICATION ENGINEERING (DECVI) /  
ADVANCED LEVEL CERTIFICATE COURSE IN  
ELECTRONICS AND COMMUNICATION  
ENGINEERING (ACECVI)**

**Term-End Examination**

00437

**June, 2014**

**BIEL-030 : DIGITAL ELECTRONICS**

*Time : 2 hours*

*Maximum Marks : 70*

---

*Note : Attempt five questions in all. Question no. 1 is compulsory.*

---

1. Choose the correct answer :  $7 \times 2 = 14$
- (a) Two's complement of the binary number 01101100 is
- (i) 10010100
  - (ii) 01101100
  - (iii) 10010011
  - (iv) 11101100
- (b) The digital operations such as AND, OR, etc. can be performed by using
- (i) switches
  - (ii) amplifiers
  - (iii) rectifiers
  - (iv) oscillators

- (c) A combinational circuit
  - (i) always contains memory elements
  - (ii) never contains memory elements
  - (iii) may sometimes contain memory elements
  - (iv) both (i) and (iii)
  
- (d) A multiplexer with 4-bit data select input is a
  - (i) 4 : 1 multiplexer
  - (ii) 8 : 1 multiplexer
  - (iii) 16 : 1 multiplexer
  - (iv) 32 : 1 multiplexer
  
- (e) A FLIP-FLOP has two outputs which are
  - (i) always zero
  - (ii) always one
  - (iii) always complementary
  - (iv) in one of the above states
  
- (f) Semiconductor memories are widely used because of
  - (i) their small size
  - (ii) their low cost
  - (iii) their compatibility with microprocessors
  - (iv) All of the above

- (g) The logic family with highest noise margin is
- (i) I<sup>2</sup>L
  - (ii) HTL
  - (iii) TTL
  - (iv) CMOS
2. (a)  $(121)_x = (100)_8$ ; find x. 7
- (b) What do you mean by Gray code ? What are its applications ? 7
3. (a) Which are the Universal gates ? Show how these can be used for realization of AND, OR and X-OR functions. 7
- (b) Prove that  $\overline{\overline{AB} + \overline{A} + AB} = 0$  7
4. Draw a 8 : 1 multiplexer circuit and discuss its working. State its use. 14
5. (a) Explain the working of JK flip-flop. 7
- (b) Enumerate the advantages and disadvantages of a ring counter. Give the circuit diagram and timing diagram for a 3-bit ring counter. 7
6. (a) With the help of neat diagram explain the working of weighted resistor type DAC. 7
- (b) What are PROMs ? Describe various methods which can be used to erase a PROM. 7

7. (a) Define following terms : 6

(i) Noise margin

(ii) Fan-out

(b) With neat circuit diagram of TTL NAND gate, explain its operation. 8

8. Write short notes on any *four* of the following :

$$4 \times 3 \frac{1}{2} = 14$$

(a) Johnson ring counter

(b) D flip-flop

(c) Shift register

(d) Comparison of different logic families

(e) SRAM

---