

**B.Tech. ELECTRICAL ENGINEERING
(BTELVI)**

**00305 Term-End Examination
June, 2014**

BIELE-004 : RF CIRCUITS

Time : 3 hours

Maximum Marks : 70

Note : Attempt any **seven** questions. Assume the missing data, if any.

1. Discuss the RF frequency behaviour of the following components : 10
 - (a) Inductor
 - (b) Capacitor
 - (c) Resistor

2. Define lossless transmission line with derivation of its input impedance. 10

3. Explain the RF models of bipolar junction transistor and pn junction diode with neat sketch. 10

4. Discuss the need of 'neutralization' in radio frequency amplifier design and explain the neutralization process with neat diagram in detail. 10

5. Discuss the low noise amplifier (LNA) topologies based on power match versus noise match in detail. 10
 6. Describe multiplier-based mixer and explain active double-balanced mixer with neat sketch. 10
 7. Describe the need of “modulation of power amplifier” process along with suitable linearization technique. 10
 8. What is resonator ? Explain the concept of quarter wave resonator used in RF oscillator design. 10
 9. Explain the approach of combination synthesizers used in RF circuits and show how it is different from direct digital synthesis method. 10
 10. Explain the working of negative resistance oscillator circuit with neat diagram. How is it different from the concepts used in ideal oscillator circuit ? 10
-