

**DIPLOMA IN ELECTRICAL ENGINEERING
(DELVI) / ADVANCED LEVEL CERTIFICATE
COURSE IN ELECTRICAL ENGINEERING
(ACELVI)**

00094

Term-End Examination

June, 2014

BIEE-027 : ELECTRICAL MACHINES – I

Time : 2 hours

Maximum Marks : 70

*Note : All questions carry equal marks. Question no. 1 is compulsory. Attempt any **four** questions out of the remaining questions.*

1. Choose the correct alternative out of the given ones. $2 \times 7 = 14$
- (a) The purpose of having a commutator and brush arrangement in a dc motor is
- (i) to produce unidirectional torque
 - (ii) to produce unidirectional current in armature
 - (iii) to help in changing the direction of rotation of the armature
 - (iv) None of the above

- (b) The number of parallel paths in the armature winding of a four-pole wave connected dc generator having 28 coil sides is
- (i) 28
 - (ii) 14
 - (iii) 4
 - (iv) 2
- (c) A dc series motor should always be started with load because
- (i) at no load it will rotate at dangerously high speed
 - (ii) at no load it will not develop high starting torque
 - (iii) it cannot start without load
 - (iv) it draws a small amount of current at no load
- (d) The core of a transformer is made of
- (i) annealed copper
 - (ii) silicon steel
 - (iii) seasoned wood
 - (iv) aluminium
- (e) The emf induced in the winding of a transformer
- (i) lags behind core flux by $\pi/2$
 - (ii) is in phase with the core flux
 - (iii) is out of phase with the core flux
 - (iv) None of the above

- (f) If the full-load copper loss of a transformer is 100 W, what will be its copper loss at half-load ?
- (i) 100 W
 - (ii) 200 W
 - (iii) 50 W
 - (iv) 25 W
- (g) Two three-phase transformers need to be connected in parallel because
- (i) the load on the transformer reduces
 - (ii) the power factor of the load increases
 - (iii) the load on the transformer increases
 - (iv) the power factor of the load decreases
2. (a) Explain why the air gap between the pole pieces and the armature is kept very small in case of a dc machine. 7
- (b) Enumerate the various losses that occur in a dc machine. 7
3. (a) Draw the power flow diagram for a dc motor and explain it. 7
- (b) The induced emf in a dc machine while running at 500 rpm is 180 V. Assuming constant flux per pole, calculate the induced emf when the machine runs at 600 rpm. 7
4. Describe how a self excited dc shunt generator builds up its terminal voltage when it is run by a prime mover. 14

5. (a) Deduce the emf equation of a transformer. 7
(b) Draw the equivalent circuit of a transformer. Show how this equivalent circuit can further be simplified without introducing much error. 7
6. The primary and secondary windings of a 30 kVA, 6000 V/230 V transformer have resistances of 10Ω and 0.016Ω respectively. The total reactance of the transformer referred to the primary side is 23Ω . Calculate the percentage regulation of the transformer when supplying full load current at a power factor of 0.8 lagging. 14
7. Explain how a 3-phase supply be converted into a 2-phase supply. Illustrate with the help of a phasor diagram. 14
8. Write short notes on any *four* of the following : $3 \frac{1}{2} \times 4 = 14$
- (i) Armature lap winding of dc machine
 - (ii) Improving commutation
 - (iii) Parallel operation of dc shunt generators
 - (iv) Testing of dc shunt motor
 - (v) Parallel operation of 3-phase transformers
 - (vi) Armature reaction
-