

**B.Tech. Civil (Construction Management) /  
B.Tech. Civil (Water Resources Engineering)**

**Term-End Examination**

**June, 2016**

00818


**ET-202(B) : PRINCIPLES OF ELECTRICAL  
SCIENCES**

*Time : 3 hours*

*Maximum Marks : 70*

*Note : Answer any five questions. Each question carries equal marks. Use of calculator is permitted.*

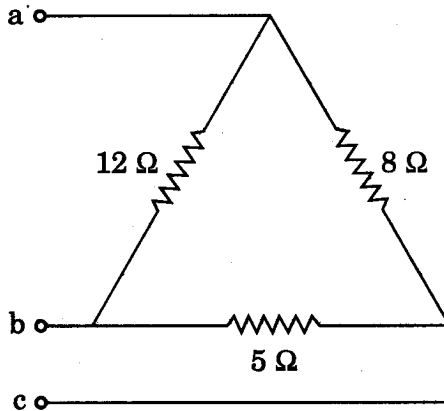1. (a) Find the equivalent star of the delta configuration shown in the following figure.



Also write the formula for converting star connection into equivalent delta.


7

(b) What are the disadvantages of low power factor in A.C. circuits? How can power factor be improved?

7

2. (a) Using Thevenin's theorem, find the current flowing through the  $1\ \Omega$  resistor. Also draw the Thevenin's equivalent circuit across the  $1\ \Omega$  resistor clearly showing the open circuit voltage.

7

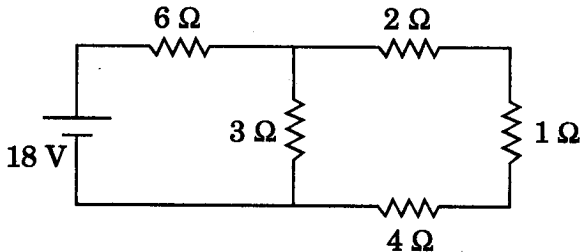

(b) Derive the relation between line current and phase current, line voltage and phase voltage for a delta connected 3-phase network.

7

3. (a) What are instrument transformers? Explain voltage and current measurement in a high voltage system with the help of instrument transformer, using connection diagrams.

7

(b) Explain the various excitation schemes for D.C. motors by providing proper circuit connection diagrams.

7

4. (a) Explain various kinds of single-phase motors and their appropriate applications.

7

(b) Explain the construction, working and application of a permanent magnet moving coil instrument.

7

5. (a) Give the circuit diagram of a Voltage Regulator with Current Booster and explain its operation. 7
- (b) Discuss the circuit, operation and principle of Peak Response type A.C. voltmeters. 7
6. (a) Discuss a basic Operational Amplifier and explain its various applications in short. 7
- (b) Give the circuit connections of a 4-bit up counter and a 4-bit down counter. Also give waveforms of each. 7
7. (a) Draw the architecture of 8085 microprocessor clearly naming its various blocks, inputs and outputs. 7
- (b) Draw the circuit of a partially decoded memory system and also draw the concerned memory map. 7
-