

**B.Tech. - VIEP - ELECTRONICS AND  
COMMUNICATION ENGINEERING  
(BTECVI)**

**Term-End Examination**

**June, 2016**

00356

**BIEL-002 : ANALOG AND INTEGRATED CIRCUITS  
DESIGN**

*Time : 3 hours*

*Maximum Marks : 70*

---

**Note :** *Attempt any seven questions. All questions carry equal marks. Missing data may be suitably assumed and mentioned. Use of scientific calculators is permitted.*

---

1. Draw the circuit diagram of a dual-input, unbalanced-output differential amplifier. Derive the expression for  $I_{CQ}$  and  $V_{CEQ}$  using DC analysis. Also derive an expression for its voltage gain, input resistance and output resistance using AC analysis. 10

2. What is the need for constant-current bias circuit in the design of differential amplifiers ? Explain the operation of a constant-current bias circuit using zener diodes with the help of a neatly labelled circuit diagram and necessary mathematical steps. 3+3+4=10

3. (a) Give the circuit diagram of a voltage-to-current converter with grounded load. Also prove that the load current ( $I_L$ ) is directly proportional to the input voltage ( $V_{in}$ ). 2+3=5
- (b) Calculate the voltage at points A and B shown in Figure 1, when  $V_1 = 5$  V and  $V_2 = 5.1$  V. Take  $R = 100$  k $\Omega$ . 5

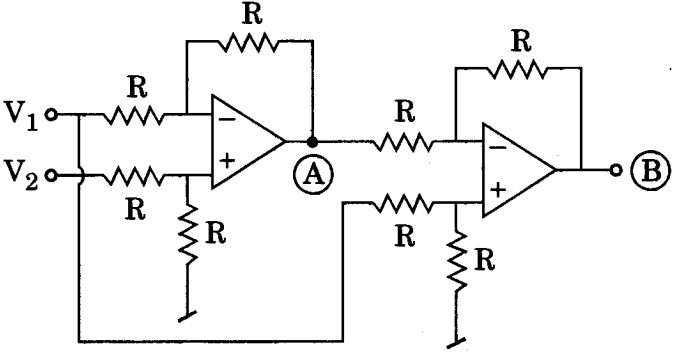


Figure 1

4. (a) Show that the circuit shown in Figure 2 is a non-inverting integrator. 5

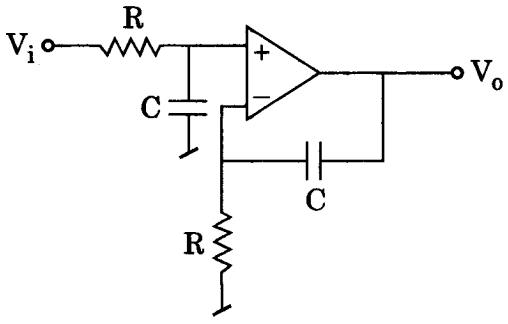


Figure 2

- (b) For the circuit shown in Figure 3, it is found that  $V_0 = a_1V_1 + a_2V_2 + a_3V_3$ . Find the values of  $a_1$ ,  $a_2$  and  $a_3$ . 5

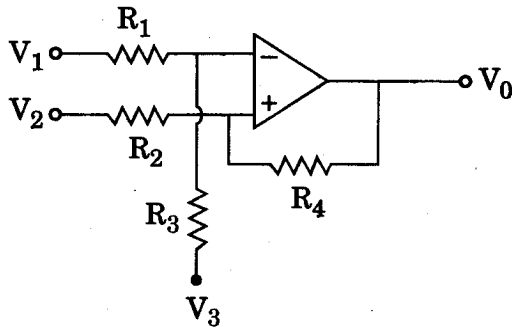


Figure 3

5. Explain the operation of a precision full-wave rectifier circuit using an op-amp with the help of neatly labelled circuit diagrams, input-output waveforms and necessary mathematical calculations. 10
6. Give the circuit diagram of a Triangular-Wave Generator that utilizes lesser number of components. Prove that the frequency of triangular-waves is given by the expression

$$f_0 = \frac{R_3}{4 R_1 R_2 C_1} \quad 10$$

7. What are regenerative comparators ? Explain their operation with the help of neatly labelled circuit diagrams and waveforms. Prove that the hysteresis voltage is given as

$$V_H = \left( \frac{2R_2}{R_1 + R_2} \right) (+ V_{sat}) \quad 10$$

8. Draw the circuit diagram of a second order Sallen-Key low pass filter. Derive an expression for its transfer function and find various filter parameters. 10
9. Define a logarithmic amplifier and give its basic diagram. What are the drawbacks of the above circuit ? How are they modified in the other form of log amplifiers ? Explain. 10
10. Write short notes on any *two* of the following :  $2 \times 5 = 10$
- (a) PLL as FSK Demodulator
  - (b) Clippers using Op-Amps
  - (c) Offset Nulling Techniques
-