

**B.Tech. – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

00806 Term-End Examination

June, 2016

BIEL-003 : DIGITAL ELECTRONICS

Time : 3 hours

Maximum Marks : 70

Note : Attempt any seven questions. All questions carry equal marks. Assume any missing data suitably.

1. (a) Design a full adder circuit using gates. 5
(b) Convert the given Boolean function into canonical SOP form : 5
$$F(A, B, C, D) = \overline{A}BC + A\overline{D} + ACD$$
2. (a) Why are asynchronous counters called ripple counters ? Explain. 5
(b) Design a half adder circuit using gates. 5
3. (a) What is the difference between static RAM and dynamic RAM ? 5
(b) Draw a ROM array and explain its working principle. 5

4. (a) Find the canonical form of the following functions : 5
- (i) $F(A, B, C) = \sum m(0, 1, 4, 7)$
- (ii) $F(A, B, C) = AB + BC$
- (b) Write a brief note on interfacing TTL with CMOS. 5
5. (a) Construct Hamming code for BCD data 0110. Use even parity. 5
- (b) Explain the concept of PAL. 5
6. Design a BCD to seven segment decoder using $2 \times 5 = 10$
- (a) PROM
- (b) PLA
7. (a) Explain the various specifications of digital ICS. 5
- (b) Convert the Gray code no. 110011 to binary. 5
8. (a) Find the value of x. 5
- $(211)_x = (152)_8$
- (b) What is meant by multiple-emitter transistor ? Explain in brief. 5
9. (a) Design a NAND gate using CMOS and explain it. 5
- (b) Subtract using r's complement. 5
- $(60)_{10} - (41.75)_{10}$

10. Write short notes on any *two* of the following : *2×5=10*

- (a) PROM
 - (b) JK flip-flop
 - (c) ASCII Code
 - (d) PRBS Generator
-