

**B.Tech. MECHANICAL ENGINEERING
(COMPUTER INTEGRATED
MANUFACTURING) /
B.Tech. (AEROSPACE ENGINEERING) (BTAE)
Term-End Examination**

June, 2016

00938

**BME-021 : PRINCIPLES OF ELECTRICAL AND
ELECTRONICS SCIENCE**

Time : 3 hours

Maximum Marks : 70

Note : Attempt *five* questions. Question no. 1 is *compulsory*. Answer any *two* questions from Section A and any *two* from Section B. Use of scientific calculator is allowed.

1. State whether the following statements are *True* or *False* : $7 \times 2 = 14$
- (a) The resistance of a conductor increases, if its length decreases.
- (b) The power consumed by a pure inductance connected to AC source is zero.

- (c) The unit of magnetic flux intensity (H) is AT/m.
- (d) The frequency of voltage at the secondary of a transformer is less than that of the primary.
- (e) BJT can be used as a switch as well as an amplifier.
- (f) Flip-flop is a basic memory element used in sequential circuits.
- (g) The barrier potential is equal to 0.7 V for silicon.

SECTION A

Attempt any *two* questions from this section.

2. (a) State and explain Kirchhoff's laws applied to DC circuits. 7
- (b) Find the resistance at 20°C of 2 km of copper wire of cross-sectional area of 0.1 cm², if the specific resistance of copper at this temperature is $17.3 \times 10^{-9} \Omega \text{ m}$. What would be its resistance at 35°C, if $\alpha = 0.0043^\circ\text{C}^{-1}$? 7
3. (a) Deduce the analogy between magnetic and electric circuits. What are the major points of difference between them? 7
- (b) State the maximum power transfer theorem. And prove that $P_{\max} = \frac{V_{\text{Th}}^2}{4R_{\text{Th}}}$ for maximum power transfer theorem. 7
4. Write short notes on the following : $4 \times 3 \frac{1}{2} = 14$
- (a) DC servomotor
- (b) Series resonance for AC circuit
- (c) Magnetic hysteresis
- (d) Quality factor

SECTION B

Attempt any two questions from this section.

5. (a) What are intrinsic and extrinsic semiconductors ? Draw and explain I – V characteristic of a diode. 7
- (b) Draw the block diagram of IC Timer 555 and its various operating modes. 7
6. (a) State the De Morgan's theorems with the help of logic gate and truth tables. 7
- (b) Write a short note on DAC and ADC. 7
7. (a) Draw the circuit of R – S flip-flop with NOR gates and discuss the behaviour of this circuit. 7
- (b) Write short notes on the following : 7
- (i) Piezo-electrical Transducers
 - (ii) MOSFET
-